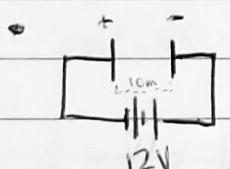


# What Electronics Deals with?

- Current (I), Electric Potential (V)
- These go through the active elements
  - Active Elements - Resistors ( $R$ )
  - Capacitors ( $C$ )
  - Inductors ( $L$ )
  - Diodes
  - Transistors

- Unit of Charge is Coulombs (C)
- Charge is quantized and the unit of charge  $1e$  is the charge of one electron
- Charge =  $q = ne$  where  $n = 1, 2, 3 \dots$
- Force =  $F = ma$  units  $\frac{\text{kg m}}{\text{s}^2}$  or N.

- Work =  $W = F \cdot d$  units  $J$  or  $\frac{\text{kg m}^2}{\text{s}^2}$
- Power =  $P_{\text{Power}} = \frac{\text{Energy}}{\text{Time}} = \frac{dW}{dt}$  units = Watts or  $\frac{\text{Joules}}{\text{second}}$
- (Coulomb) Force =  $F_c = \frac{kq_1 q_2}{r^2}$   $k = \frac{1}{4\pi\epsilon_0}$   $\epsilon_0$  is permittivity of free space =  $8.82 \times 10^{-12} \frac{\text{C}^2}{\text{N}^2 \text{m}^2}$
- Electric Field =  $\vec{E} = \frac{\vec{F}}{q} = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2}$  units =  $\frac{N}{C}$
- Voltage or Potential Difference  $dV = \frac{dW}{q} = \vec{E} \cdot \vec{d}$   $V = -\int \vec{E} \cdot d\vec{l}$ 
  - Units of Voltage =  $\frac{W}{C} = V$  (volts)  $(J/C)$



$$\Delta V = \vec{E} \cdot \vec{d}$$

$$\Delta V = E \cdot d$$

$$12 - \vec{E}$$

$$12 - E$$

$$12 - E$$

$$f = ma$$

$$F = qE$$

$$F = (1.6 \times 10^{-19})(1200)$$

$$F = 1.9 \times 10^{-16} N$$

$$ma = 1.9 \times 10^{-16}$$

$$a = \frac{1.9 \times 10^{-16}}{9.11 \times 10^{-31}}$$

$$a \approx 2 \times 10^{14} \frac{m}{s^2}$$

negative ends to make work positive

Perriver  $AE = \frac{\Delta V}{\Delta t}$  receives a  $\frac{1 \text{ mV}}{1 \text{ m}}$  field

~~AE~~ ~~area~~  
antenn.

$$\Delta V = \Delta E = Ad$$

$$\Delta V = 1 \text{ mV} \cdot 1 \text{ m}$$

$$\Delta V = 1 \text{ mV} \approx 0.001 \text{ V}$$

- Current - the time rate at which charge  $Q$  pass a given cross section in time,  $t$ .

$$- I = \frac{\Delta Q}{\Delta t} = \frac{C}{S} = \text{Amps.}$$

$$\bullet \text{Power} = \frac{\Delta W}{\Delta t} \rightarrow \frac{\Delta W}{\Delta t} \cdot \frac{\Delta Q}{\Delta t} = V \cdot I = VI$$

- ~~W~~ Resistor ~~W~~ - Inductor
- ~~I~~ Capacitor ~~B~~ - Battery


$$\bullet \text{Ohms Law. } R = \frac{\Delta V}{I} \text{ in } \Omega \quad R = \rho \cdot \frac{L}{A} \quad \rho = \text{resistivity in } \Omega \cdot \text{m}$$

~~A~~ = ~~length~~ ~~A~~ = ~~area~~

- Battery - Chemical Energy converted to electrical energy

- Ideal battery has no internal resistance.

- " " " has constant voltage.

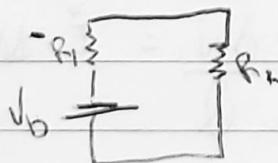

$$V_B = R_1 I + \frac{R_2}{V_L}$$

$$V_L = V_B - R_1 I$$

$$I = \frac{V_B}{R_2 + R_1}$$

$$V_L = I R_2 = \frac{V_B}{1 + \frac{R_2}{R_1}} \quad R_2 = 10$$

$$V_L = V_B$$


$$V_B = R_1 I + R_2 I$$

Joule's Heating Law:  $P = VI$



$$= \frac{V^2}{R} = R_1 I^2$$

$$\int dQ = Q = \int_{t_1}^{t_2} P dt$$

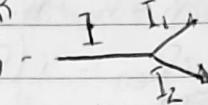Kirchhoff's Current Law -  $I_1 + I_2 = I$




$$\text{Zener Law: } V_B = V_P + V_D$$

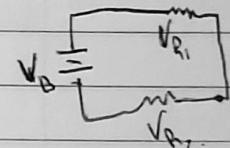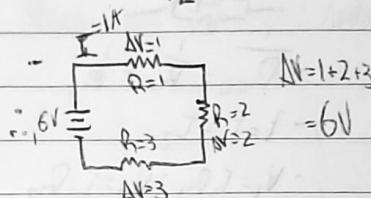

- In any closed loop, potential energy is equal to zero.

Example:

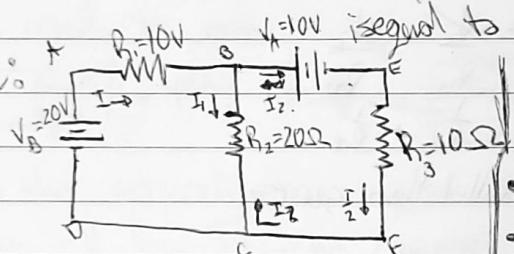

$$\text{Loop ABCDA: } -R_1 I - R_2 I_1 + V_B = 0$$

$$-10I - 20I_1 + 20 = 0$$

$$V_{AB} = -R_1 I \quad (\text{from A to B})$$

$$V_{ACB} = +R_1 I \quad (\text{from A to C})$$

$$A \xrightarrow{I} C \xrightarrow{I_1} B$$

$$V_{AB} = -V$$

$$V_{BA} = V$$

$$\text{Loop BEFCB: } -10V - 10I_2 + 20I_1 = 0$$

$$I - I_1 - I_2 = 0$$

$$\begin{cases} -10I + 20I_1 = 20 \\ -10I_2 + 20I_1 = 10 \\ I = I_1 + I_2 \end{cases}$$

$$I_1 = 3A$$


$$I_2 = 5A$$

$$\begin{cases} -10I_1 - 10I_2 + 20I = 0 \\ -10I_2 + 20I_1 = 10 \end{cases}$$

Easier Way:  $20V = 10I_1 + 20I_1 - 20I_2$


$$-10V = 10I_2 + 20I_2 - 20I_1$$

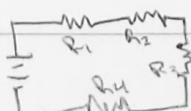Voltage Divider (Resistors in Series) -  $V_{R_3} = \frac{R_3}{R_1 + R_2 + R_3 + R_4} \cdot V$



- Add all resistors in denominator. Voltage across one resistor with voltage.

• Resistor in Series and Parallel.

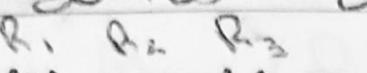- Series - 

-  $R_{EQ} = R_1 + R_2 + R_3$ .

-  $V_{EQ} = i R_{EQ} = i (R_1 + R_2 + R_3)$ .

- Parallel - 

-  $\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$ .

-  $I = I_1 + I_2$

-  $V_1 = I_1 R_1; V_2 = I_2 R_2$

~~-  $\Delta V = V_1 + V_2 = I_1 R_1 + I_2 R_2$~~   $\Delta V = I R_{EQ}$


~~-  $\Delta V = \Delta V_1 + \Delta V_2$~~

$R_{EQ} \quad R_1 \quad R_2$

$= \frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2}$


• Solve parallel then series.

# Voltage Source vs Current Source

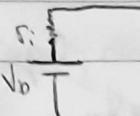- Voltage Source -  battery is the voltage source here.
- Current Source -  Used when a constant current is needed.

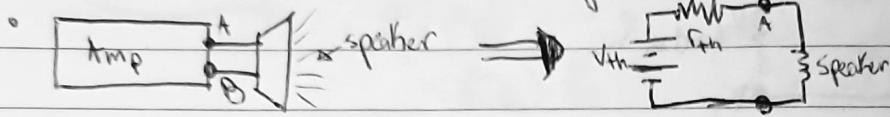
## Network Simplification

- This is used to make complicated circuits simple



- We say this network has equivalent resistance and voltage which we call the Thevenin Equivalent.

- Example:

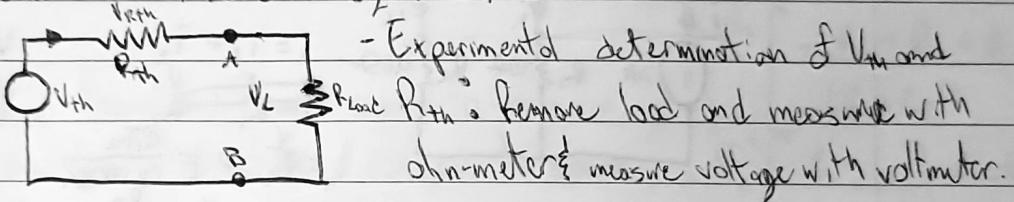


$$V_{th} + V_{A\text{th}} + V_L = 0$$

$$V_{th} - iR_{th} - V_L = 0$$

$$V_L = V_{th} - iR_{th}$$

$$\text{When } i=0, V_L = V_{th}$$

$$\text{When } V_L=0, V_{th}=iR_{th}$$

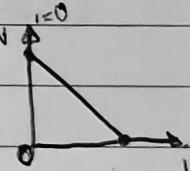

- Theoretical Calculation of  $V_{th}$  &  $R_{th}$

-  $V_{th}$  - Remove the load and measure the potential difference from A-B

-  $R_{th}$  - To determine  $R_{th}$ , one short circuit the voltage circuit, then calculate the equivalent resistor of the circuit.

- Find the Thevenin Equivalent of the following circuit ( $V_{th}$  &  $R_{th}$ )



$$V_{AB} = V_{th}$$

$$V_A = V_{B\text{th}} \cdot \frac{R_B}{R_A+R_B}$$

$$V_B = V_{B\text{th}} \cdot \frac{R_A}{R_A+R_B}$$

$$V_{th} = V_A - V_B \quad R_{th} = R_{eq1} + R_{eq2}$$

$$V_A = 2 \cdot \frac{3}{4}$$

$$V_A = \frac{3}{2}$$


$$V_B = 2 \cdot \frac{4}{5}$$

$$V_B = \frac{4}{3}$$

$$V_{th} = \frac{1}{6} \text{ V}$$



$$R_{th} = \frac{25}{12} \Omega$$

# Example

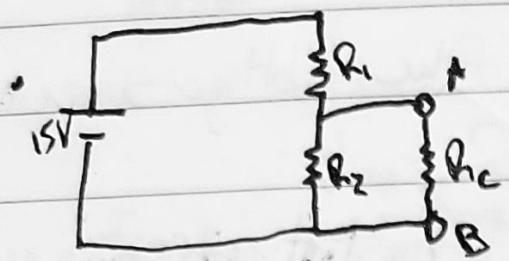


Find Thevenin Egnir.
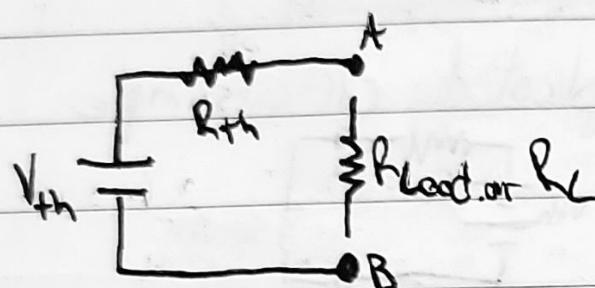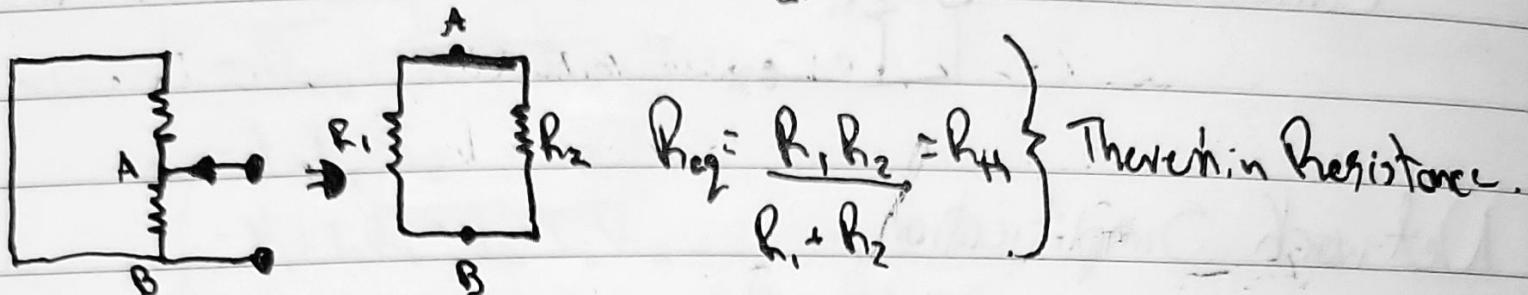
$$V_{AB} = \frac{V_{R_2}}{R_1 + R_2} = V_{th} \quad \left. \right\} \text{Thevenin Voltage}$$



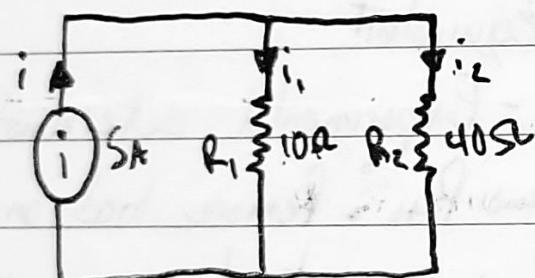Determine the current through both resistors



$$i = i_1 + i_2$$

$$i = \frac{V}{R_1 + R_2}$$

$$i_1 = \frac{V}{R_1} \Rightarrow i_1 = \frac{i R_1}{R_1 + R_2}$$

$$i_1 = i \frac{R_1}{R_1 + R_2}$$

$$V = i R_{eq} \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V = i \frac{R_1 R_2}{R_1 + R_2}$$

$$i_2 = \frac{i R_2}{R_1 + R_2}$$


$$i = \frac{i R_2}{R_1 + R_2} + \frac{i R_1}{R_1 + R_2}$$

$$\frac{R_1 + R_2}{R_1 + R_2}$$
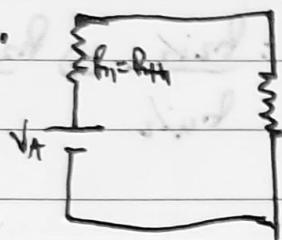
# Maximum Power Transfer



- We want to connect a load to the network, what should be the network resistance (impedance) in order to have the maximum power transfer to the load?



$$P = \frac{V^2}{R} = I^2 R = V_A^2 / (R_1 + R_2)$$

$$\begin{aligned} P &= I^2 R_2 \\ &= \left(\frac{V_A}{R_1 + R_2}\right)^2 R_2 \\ &= \frac{V_A^2 R_2}{(R_1 + R_2)^2} \end{aligned}$$

$$I = \frac{V_A}{R_1 + R_2}$$

$$y = f(x) \rightarrow \frac{dP}{dx} = V_A^2 \left[ \frac{2R_2}{(R_1 + R_2)^3} + \frac{1}{(R_1 + R_2)^2} \right]$$



$$\begin{aligned} y' &= f'(x) \quad \frac{dP}{dx} \\ &= V_A^2 \left[ \frac{-2R_2}{(R_1 + R_2)^3} + \frac{1}{(R_1 + R_2)^2} \right] \\ &= V_A^2 \left[ \frac{-2R_2 + R_1 + R_2}{(R_1 + R_2)^3} \right] \end{aligned}$$

The  $P_{max}$  transfers from source to load

when the load resistance is equal to source  $= V_A^2 / (R_1 + R_2)$

$$P = i_2 R_L = \frac{V^2}{4R_L}$$

- Power Transfer Graphically

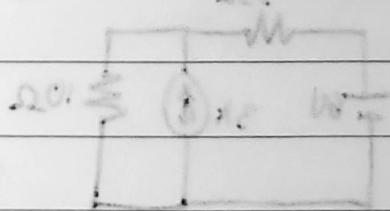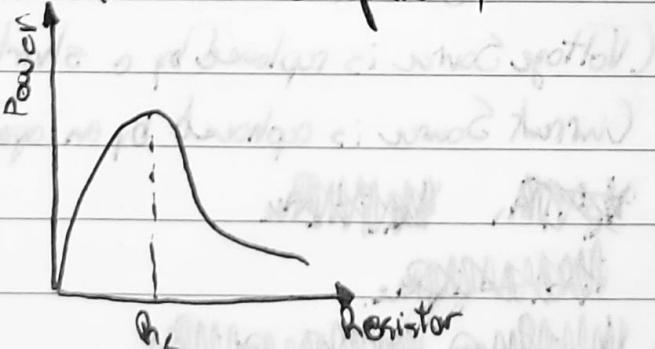

# The Wheatstone Bridge.

Ammeter



- $R_{\text{var}}^*$  is a variable resistor

- We change  $R_{\text{var}}$  till no current flows through ammeter  
 $\Rightarrow i_2 = 0, i_3 = i$

- Potential across  $\square$ ,  $V_{CD} = V_{\text{Battery}}$ .


- $V_B - V_C = V_B - V_D$

$$\frac{R_1}{R_2} i_1 = \frac{R_2}{R_3} i_2 \Rightarrow \frac{R_1}{R_2} = \frac{R_2}{R_3} \Rightarrow R_3 = \frac{R_1 R_2}{R_2}$$

$$R_3 i_1 = R_4 i_2 \quad R_3 = \frac{R_4 i_2}{i_1}$$

## Solving Complex Circuits


Current Source

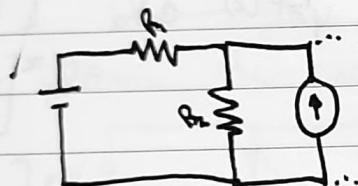

Q: Measure current through  $R_2$ .

- Superposition Principle: Tells us that one can solve a network problem by shutting off all sources with the exception of one. Solve the problem for this source, then continue for all other sources. Finally, add up the results of all the sources.

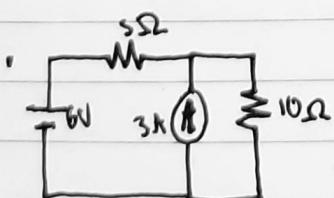(Voltage Source is replaced by a short circuit,  
 Current Source is replaced by an open circuit)



$$V = V_1 + V_2$$

$$6 = i R_1 + i R_2 \quad V_5 = V_{10}$$

$$6 = i S$$

$$\frac{6}{S} = i_1$$

$$i_1 R_3 = i_2 R_{10}$$

$$i_1 = i_2 \cdot 2$$

$$i_1 + i_2 = i \Rightarrow i_1 = 2(3) - 2i_1 \Rightarrow i_1 = 2i_1$$

$$V_1 = V_{10} = 6$$

$$= 2 - \frac{6}{15}$$

$$= \frac{30}{15} - \frac{6}{15} \Rightarrow \frac{24}{15} = \frac{8}{5} \Rightarrow 1.6 \Omega$$


## Example

- A resistor at  $20^\circ\text{C}$   $R(20) = 1000 \Omega$ . What is the resistance at  $100^\circ\text{C}$ ?  $\alpha_c = -0.0005 \frac{\Omega}{^\circ\text{C}}$  ( $\alpha_c$  is the coefficient of thermal conductivity).

$$R = R_0 (1 + \alpha \Delta T)$$

$$= 1000 (1 + (-0.0005)(80))$$

$$= 960 \Omega$$

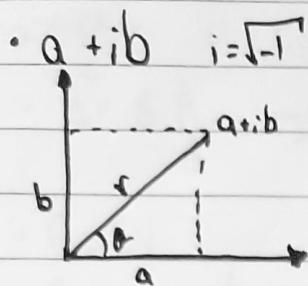

$$a+ib = r(\cos\theta + i\sin\theta) = re^{i\theta}$$

$$\theta = \arctan\left(\frac{b}{a}\right) \quad r = \sqrt{a^2+b^2}$$

$$\frac{1}{a+ib} = \frac{1}{a+ib} \cdot \frac{a-ib}{a-ib} = \frac{a-ib}{a^2+b^2}$$

•  $\sin^2\theta + \cos^2\theta = 1$

$$\cos 2\theta = \cos^2\theta - \sin^2\theta$$

$$\sin 2\theta = 2\sin\theta\cos\theta$$

$$= 2\cos^2\theta - 1$$

$$= 1 - 2\sin^2\theta$$

•  $f(\theta) = \sin\theta \quad f'(\theta) = \cos\theta$


$$f(\theta) = \cos\theta \quad f'(\theta) = -\sin\theta$$

$$f(\theta) = \tan\theta \quad f'(\theta) = \sec^2\theta$$
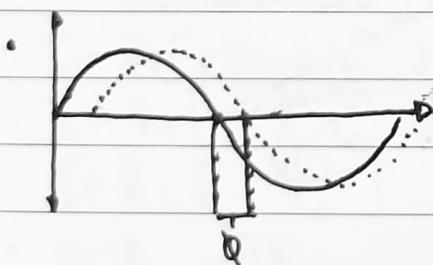
## AC Circuits



$$V = V_0 \sin(\omega t) \quad \omega = 2\pi f \Rightarrow 2\pi \frac{1}{T} \left( \frac{\text{rad}}{\text{s}} \right)$$



$$V = V_0 \sin(\omega t - \phi)$$



$$V = V_0 \sin(\omega t - \phi) \quad \omega = \frac{2\pi}{T} = 0.63$$

$$V = V_0 \sin(\omega t - \phi) \quad V = V_0 \sin(\omega t - \phi)$$

$$10 = 10 \sin(0 - \phi) \quad \rightarrow V = 10 \sin(0.63t + \frac{\pi}{2})$$

$$10 = 10 \sin(-\phi)$$

$$-\frac{\pi}{2} = \phi$$

# Resistor in AC Circuit.

$$\bullet R = \frac{V}{I} \quad R = \rho L$$

$$\bullet \text{Series} \rightarrow \text{freq} = f_1 + f_2 + f_3 \dots$$

$$\text{Parallel} \rightarrow \frac{1}{\text{freq}} = \frac{1}{f_1} + \frac{1}{f_2} + \frac{1}{f_3} \dots$$

$$\bullet V = V_s \sin(\omega t)$$

$$\frac{V}{R} = \frac{V_s}{R} \sin(\omega t)$$



$$I = I_s \sin(\omega t)$$

$$\bullet P(t) = \frac{V_s^2}{R} (1 - \cos 2\omega t)$$

$$\therefore \int P(t) dt = \int \frac{V_s^2}{R} \left( \frac{1}{2} - \cos 2\omega t \right) dt$$

$$W = \frac{V_s^2}{R} \left[ \frac{1}{2} - \frac{1}{2} \sin 2\omega t \frac{1}{2\omega} \right]$$
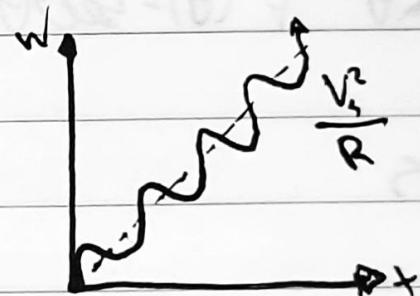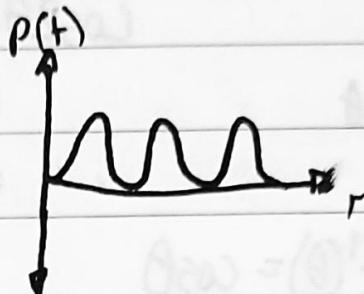
$$W = \frac{V_s^2}{R} \left[ \frac{1}{2} - \frac{1}{2} \sin t \right]$$



$$\bullet \overline{P(t)} = \frac{V_s^2}{2} \cdot I_s$$

$$\sqrt{P_{\text{rms}}} = \frac{V_s}{\sqrt{2}}$$

$$\frac{1}{T} \int_{0 \text{ to } T} P(t) dt = \frac{V_s^2}{R}$$

$$\overline{P(t)} = \sqrt{P_{\text{rms}}} I_{\text{rms}} = \frac{\sqrt{V_s} I_s}{2}$$

## Capacitors in AC Circuit

- $\frac{1}{C} = \frac{1}{f}, f, \text{mF} = 10^{-3} \text{F}, \mu\text{F} = 10^{-6} \text{F}, \text{nF} = 10^{-9} \text{F}, \text{pF} = 10^{-12} \text{F}$
- $C = \frac{\epsilon A}{d}$    $\epsilon_0 = \epsilon_0 \epsilon_r$ ,  $A = \text{area of plates}$ ,  $d = \text{distance between the capacitors}$ .

$$Q = CV$$

$$\text{Series} \rightarrow \frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} \dots$$

$$\text{Parallel} \rightarrow C_{\text{eq}} = C_1 + C_2 \dots$$


$$\text{Circuit Diagram: } \text{AC Source} \parallel \text{Capacitor} \frac{1}{C}$$

$$i = \frac{dQ}{dt} = \frac{d(CV)}{dt} = C \frac{dV}{dt} = C \frac{dV \sin(\omega t)}{dt}$$

$$= CV_s \cos(\omega t) \omega$$

$$= C \omega V_s \cos(\omega t)$$
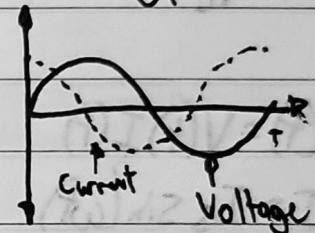
$$i = C \omega V_s \sin(\omega t + \frac{\pi}{2})$$



## Capacitive Reactance

$$V = V_s \cos(\omega t) = \text{Re}[V_s e^{i\omega t}]$$

$$I = C V_s \omega \cos(\omega t + \frac{\pi}{2})$$

$$I = \text{Re}[C V_s \omega e^{i\omega t + \frac{\pi}{2}}]$$

$$I = \text{Re}[C V_s \omega i e^{i\omega t}]$$

$$I = \text{Re}\left[\frac{CV_s e^{i\omega t}}{i\omega C}\right]$$

$$I = \text{Re}\left[\frac{V(t)}{X_C}\right]$$

$$V = IR$$

$$V = I X_C \text{ where } X_C = \frac{1}{i\omega C}$$

# Inductors in AC Circuits

$$\text{Inductance } L = \frac{\Phi}{I} \quad [\text{Wb}] \text{ H}$$

$$V = \frac{d\Phi}{dt} \quad \Phi = \int_0^t V dt \quad I = \frac{\Phi}{L}$$

$$I = \frac{\Phi}{L} = \frac{1}{L} \int_0^t V dt = \frac{1}{L} \int_0^t \sqrt{s} \cos(\omega t) dt = \frac{\sqrt{s}}{L} (\sin(\omega t)) \Big|_0^t$$

$$I = \frac{\sqrt{s}}{L} \sin(\omega t) = \frac{\sqrt{s}}{\omega L} \cos(\omega t - \frac{\pi}{2})$$

$$P(t) = V(t)I(t) \quad V = \frac{d\Phi}{dt} \quad L = \frac{\Phi}{I}$$

$$I = I_s \sin(\omega t)$$

$$V = \frac{d(I_s)}{dt}$$

$$V = \frac{d(I_s \sin(\omega t))}{dt}$$

$$V = L I_s \omega \cos(\omega t)$$

$$W = \int_0^t P(t) dt = \int_0^t V(t) I(t) dt$$

$$W = L \int_0^t I_s \omega \cos(\omega t) dt$$

$$W = \frac{L I_s^2}{2}$$

# Inductors Reactance

$$V = V_0 \cos(\omega t) \quad V = \frac{d\Phi}{dt} \quad L \cancel{\frac{d\Phi}{dt}} \quad I = \Phi = \frac{1}{L} \int_0^t V dt = \frac{1}{L} \int_0^t V_0 \cos(\omega t) dt$$


$$I = \frac{V_0}{\omega L} \sin(\omega t) = \frac{V_0}{\omega L} \sin(\omega t - \frac{\pi}{2}) = \frac{-V_0}{\omega L} \cos(\omega t - \frac{\pi}{2})$$

$$I = \text{Re} \left[ \frac{V_0}{\omega L} e^{i\omega t} \right] \quad I = \text{Re} \left[ \frac{V_0}{\omega L} \right]$$

$$I = \text{Re} \left[ \frac{V_0}{\omega L} e^{i\omega t} \right]$$

$$I = \text{Re} \left[ \frac{V(t)}{X_L} \right]$$

$$V = IR \quad V = I X_L$$

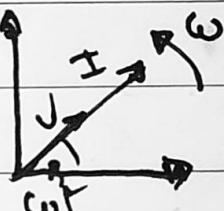


$$V = I X_L \quad X_L = \frac{1}{i\omega C}$$

$$V = I X_L \quad X_L = i\omega L$$

## R<sub>C</sub> Filters

### • Lowpass R<sub>C</sub> Filter

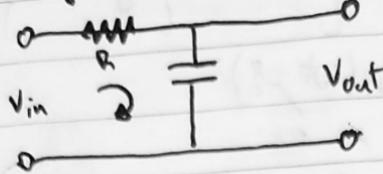

$$V_{in} = IR + V_{out}$$

$$V_{in} = IR + \frac{I}{i\omega C}$$

$$V_{in} = I(R + \frac{1}{i\omega C})$$

$$\frac{V_{in}}{R + \frac{1}{i\omega C}} \approx 1$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega RC + 1}$$

$$a = 1$$

$$b = j\omega RC$$

$$\omega_0 = \frac{1}{RC}$$


$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$= \frac{1}{1 + \omega^2 R^2 C^2}$$

↓

$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j\theta}$$
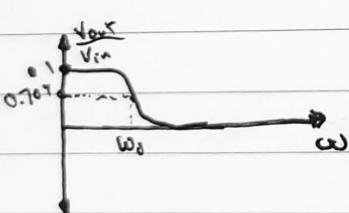
$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} e^{j\theta}$$




$$\omega = 0 \quad \frac{V_{out}}{V_{in}} = 1$$

$$\omega = \omega_0 \quad \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\omega > \omega_0 \quad \frac{V_{out}}{V_{in}} = 0$$
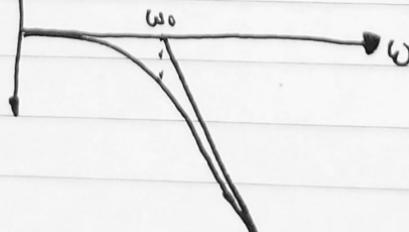
### Power Gain

$$\frac{P_2}{P_1} = 10 \log \omega \Rightarrow \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2}{V_1} = 20 \log_{10} \frac{V_2}{V_1}$$



$$\left| \frac{V_{out}}{V_{in}} \right|^2 = \left| \frac{V_{out}}{V_{in}} \right| \cdot \left| \frac{V_{out}}{V_{in}} \right|$$


$$= \frac{1}{1 + \frac{1}{1 - i\omega RL}}$$

$$= \frac{1 - i\omega RL}{1 + i\omega RL}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{\frac{\omega}{\omega_0}}}$$

# High Pass RC Filter

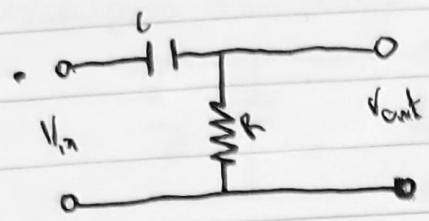

$$V_{in} = \frac{I}{i\omega C} + V_{out} \Rightarrow I = \frac{V_{in}}{i\omega C}$$

$$V_{in} = I \left( \frac{1 + R}{i\omega C} \right)$$

$$I = \frac{V_{in}}{\frac{1}{i\omega C} + R}$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + i\omega C}$$

$$= \frac{\frac{V_{in}}{R}}{\frac{1}{i\omega C} + R} \cdot R$$

$$= \frac{R}{\frac{1}{i\omega C} + R}$$

$$\frac{V_{out}}{V_{in}} = \frac{i\omega RL}{1 + i\omega RL} \cdot \frac{1 - i\omega RC}{1 - i\omega RC}$$

$$= \frac{i\omega RL + \omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}$$

$$= \frac{\omega RL(i + \omega RC)}{1 + \omega^2 R^2 C^2}$$

$$\frac{V_{out}}{V_{in}} = \frac{\omega RL}{1 + \omega^2 R^2 C^2} \sqrt{1 + \omega^2 R^2 C^2} e^{j\theta}$$

$$= \frac{\omega RL}{\sqrt{1 + \omega^2 R^2 C^2}} \cdot e^{j\theta}$$

$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \cdot e^{j\theta}$$



$$= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \cdot e^{j\theta}$$

$$\left| \frac{V_{out}}{V_{in}} \right|^2 = \left| \frac{-i\omega RC}{1 - i\omega RC} \right| \cdot \left| \frac{i\omega RL}{1 + i\omega RL} \right|$$


$$= \frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}$$

$$= \frac{1}{1 + \frac{1}{\omega^2 R^2 C^2}}$$
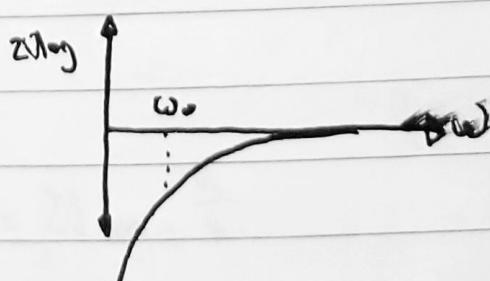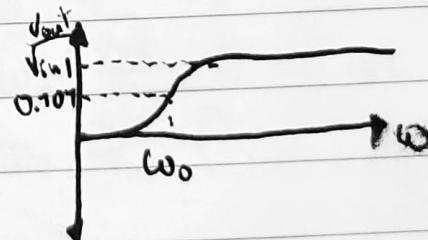
$$= \frac{1}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}}$$



# RLC Circuits

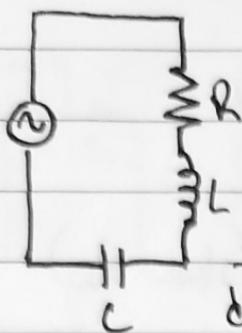

$$V = V_0 \cos(\omega t)$$

$$V = IR + Ii\omega L + \frac{I}{i\omega C}$$

$$V = IR + L \frac{dI}{dt} + \frac{I}{C}$$

$$\frac{d}{dt}(V_0 \cos(\omega t)) = IR + L \left( \frac{dI}{dt} - \frac{I}{C} \right)$$

$$-V_0 \sin(\omega t) = R \frac{dI}{dt} + L \frac{d^2 I}{dt^2} + \frac{1}{C} \frac{dI}{dt}$$

$$-V_0 \sin(\omega t) = R \frac{dI}{dt} + \left( \frac{d^2 I}{dt^2} + \frac{1}{C} I \right)$$

$$I = I_0 \cos(\omega t)$$

$$I = V_0 \cos(\omega t)$$

$$R + i(\omega L + \frac{1}{\omega C})$$

$$= R \cdot \frac{\sqrt{}}{R + i(\omega L + \frac{1}{\omega C})} \cdot \frac{R - i(\omega L - \frac{1}{\omega C})}{R - i(\omega L - \frac{1}{\omega C})}$$


$$= \frac{\sqrt{(R - i(\omega L - \frac{1}{\omega C}))}}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}{R^2 + (\omega L - \frac{1}{\omega C})^2} e^{i\theta}$$

$$= \frac{\sqrt{}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{i\theta}$$


$$X_C X_L Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

b)

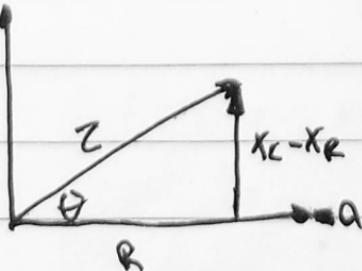

# RLC in Series

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

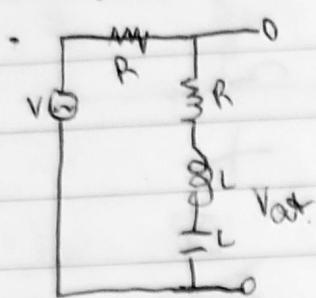

$$V_{in} = V_R + V_L + V_C$$

$$V_{in} = iR_1 + iR_2 + iX_L + iX_C$$

$$\frac{V_{in}}{V_{out}} = \frac{iR_1 + iR_2 + iX_L + iX_C}{iR_1 + iX_L + iX_C}$$


$$\frac{V_{in}}{V_{out}} = \frac{R_1 + X_L + X_C}{R_1 + R_2 + X_L + X_C}$$

$$\frac{V_{in}}{V_{out}} = \frac{R_1 + i(\omega L - \frac{1}{\omega C})}{R_1 + R_2 + i(\omega L - \frac{1}{\omega C})}$$

$$\frac{V_{in}}{V_{out}} = \frac{R_1}{R_1 + R_2}$$


$$X_L + X_C = i(\omega L + \frac{1}{\omega C})$$
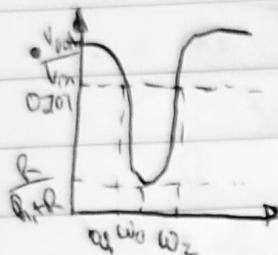
$$\Delta\omega = \omega_2 - \omega_1 = B = \text{Bandwidth.}$$



• Q = Quality Factor
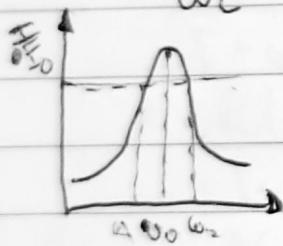
$$Q = 2\pi \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\Delta\omega}$$



## Admittance

$$Y = \frac{1}{Z} = \frac{1}{R + j\omega L + j\omega C}$$

$$Y = \frac{1}{R} + j\omega L + j\omega C$$

$$Y = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$$

$$Y = \frac{G + jB}{G^2 + B^2}$$

G = Conductance

B = Susceptance.

Example

$$I = I_1 + I_2$$


$$\frac{V}{Z} = \frac{V}{R + jX_L} + \frac{V}{jX_C}$$

$$\frac{1}{Z} = \frac{1}{R + j\omega L} + j\omega C$$

$$Y = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$Y = j\omega C + \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega C}{R^2 + \omega^2 L^2}$$
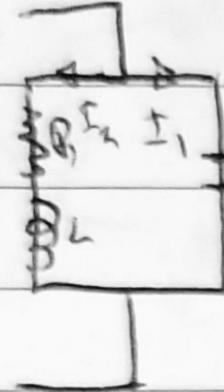
$$Y = \frac{R}{R^2 + \omega^2 L^2} + j\left[\omega C - \frac{\omega L}{R^2 + \omega^2 L^2}\right]$$



$$f_0 = 20$$

$$L = 1 \text{ mH}$$


$$C = 1 \text{ nF}$$

$$Z_0 = ? \quad \omega = \omega_0$$

$$Z_0 = 50.0 \Omega \text{ KSL}$$

# Power Factor

$\cdot RLC$

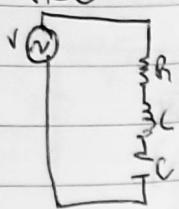


$$\overline{P(t)} = V_{rms} I_{rms} \cos(\phi)$$

Power factor


$$\overline{P(t)} = V_{rms} I_{rms} \frac{R}{Z}$$

$$V_R \Rightarrow \phi = 0 \quad \cos(0) = 1 \Rightarrow \bar{P} = \max$$

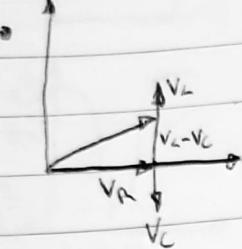
$$V_{L or C} \Rightarrow \phi = \pm \frac{\pi}{2} \quad \cos(\pm \frac{\pi}{2}) = 0 \Rightarrow \bar{P} = 0$$


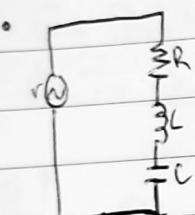
$$I = \frac{V_0 e^{i\omega t}}{R + i\omega L + i\omega C} = I_0 e^{i\omega t}$$


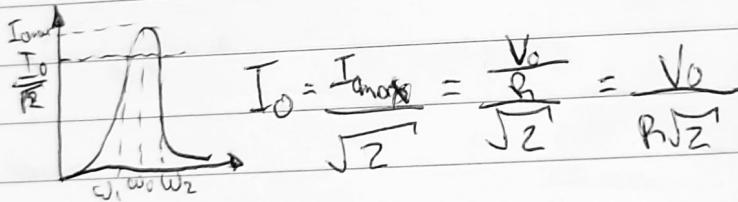
$$I_0 = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\omega_2 - \omega_1}$$



Example

$\cdot$   $V = \text{Re}[e^{i2t}] = \text{Re}[e^{i0}] = 1$   $I = 2I_1 - iI_1 + I_2$   $\tan^{-1}\left(\frac{-1}{2}\right) = \frac{\pi}{4}$

$$X_L = i\omega L = 2i$$

$$X_C = \frac{1}{i\omega C} = \frac{1}{i(2)(\frac{1}{2})}$$

$$X_E = -i$$

$$V = \text{Re}[V_2 e^{i\omega t}]$$

$$= \text{Re}[R_2 I_2 e^{i2t}]$$

$$I = I_1 + I_2 \quad (1)$$


$$= \text{Re}\left[\frac{R_2}{2} e^{i(2t + \frac{\pi}{4})}\right]$$

$$0 = -iI_2 + 2I_2 + iI_1$$


$$0 = iI_1 + (2 + i)I_2 \quad (2)$$

$$(1) - (2) = 2iI_2 + 2I_2$$

$$I_2 = \frac{1}{4}(-1 - i)$$

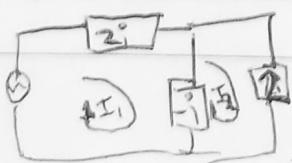

Exemple

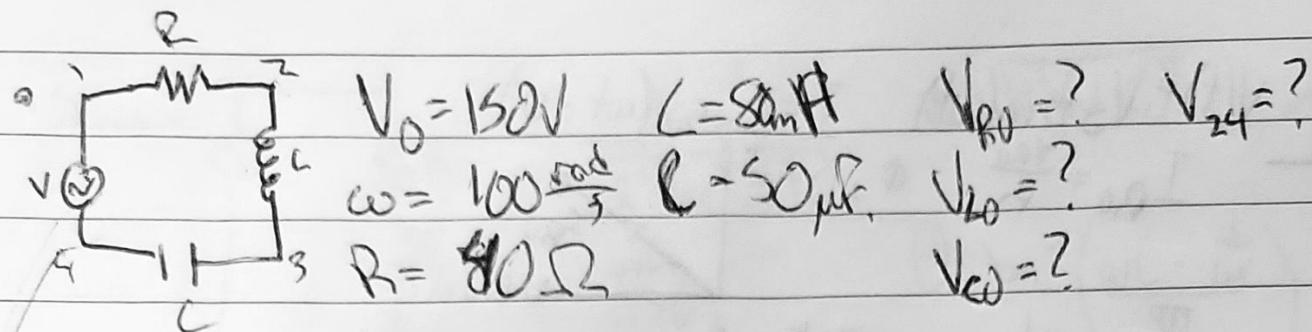

$$X_L = \omega L = (100)(80) \cdot 10^{-3} = 8\Omega$$
$$Z = \sqrt{R^2 + (8-200)^2} = 196.12\Omega$$
$$X_C = \frac{1}{\omega C} = \frac{1}{(100)(50) \cdot 10^{-6}} = 200\Omega$$

$$I_0 = \frac{V_0}{Z} = \frac{150}{196.12} = 0.765A$$
$$V_{R0} = RI_0 = 30.6V$$
$$V_{L0} = X_L I_0 = 6.12V$$
$$R \times V_{C0} = X_C I_0 = 153V$$

$$V_{24} = 6.12 + 153 \\ = 146.88V.$$

$$R = 80\Omega \quad V_0 = 40V$$
$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = 43.86\Omega$$
$$L = 160\text{mH} \quad \omega = 200 \frac{\text{rad}}{\text{s}}$$
$$C = 100\mu\text{F} \quad Z = ?$$


$$I_0 = \frac{V_0}{Z} = 0.912A$$

$$\tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right) = -24.2^\circ$$
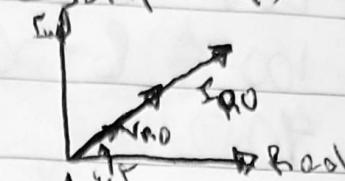
# Summary

• AC  $V(t) = V_s \sin(\omega t)$   $I = I_s \sin(\omega t - \phi)$

•  $\text{---} \frac{1}{R}$   $I_{R0} = \frac{V_{R0}}{R}$   $\phi = 0$



•  $\text{---} i$   $I_{C0} = \frac{V_{C0}}{X_C}$   $\phi = -\frac{\pi}{2}$




•  $\text{---} m$   $I_{L0} = \frac{V_{L0}}{X_L}$   $\phi = +\frac{\pi}{2}$





$$V = \frac{d\phi}{dt}, L = \frac{\phi}{I}$$

$$V = \frac{d(LI)}{dt} = L \frac{dI}{dt}$$


## RC Filters

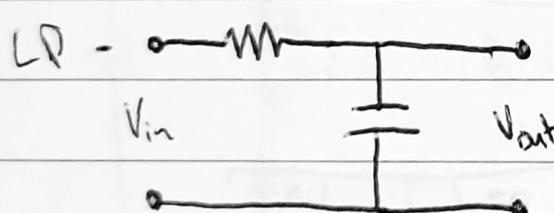
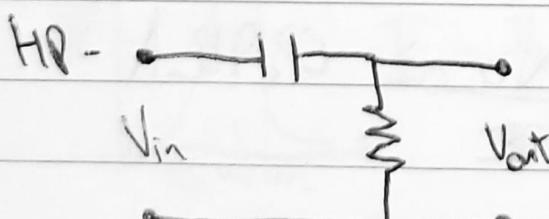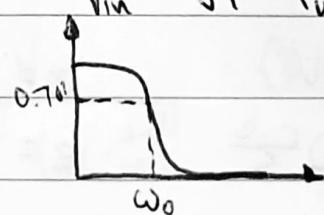
$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \cdot e^{j\theta} \quad \theta = \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$



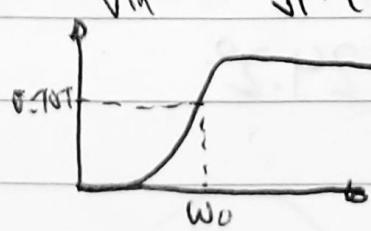
$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + (\frac{\omega_0}{\omega})^2}} \cdot e^{j\theta} \quad \theta = \tan^{-1}\left(\frac{\omega_0}{\omega}\right)$$




# RLC Circuit

\* Series -

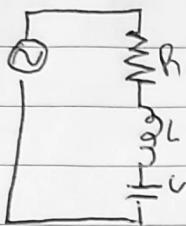


$$I = \frac{\sqrt{c} e^{i\theta}}{\sqrt{R^2 + (wL - \frac{1}{wC})^2}}$$
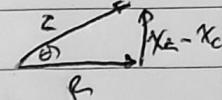
$$Z = \sqrt{R^2 + (wL - \frac{1}{wC})^2}$$



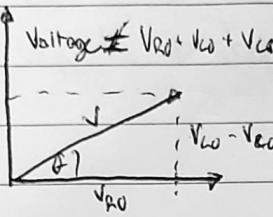
$$\theta = \tan^{-1} \left( \frac{wL - \frac{1}{wC}}{R} \right)$$



$$V = \sqrt{V_{R0}^2 + (V_{L0} - V_{C0})^2}$$

\* Parallel -

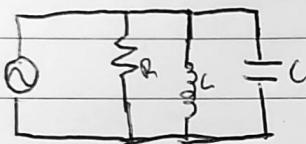


$$I(t) = I_{R0} \sin(\omega t) + I_{L0} \sin(\omega t + \frac{\pi}{2}) + I_{C0} \sin(\omega t - \frac{\pi}{2})$$



$$I_{\parallel} = \sqrt{I_{R0}^2 + (I_{C0} - I_{L0})^2}$$

$$Z = \sqrt{\frac{1}{R^2} + \left( \frac{1}{X_C} - \frac{1}{X_L} \right)^2} \quad \theta = \tan^{-1} \left( R \left( \frac{1}{X_C} - \frac{1}{X_L} \right) \right)$$

Example

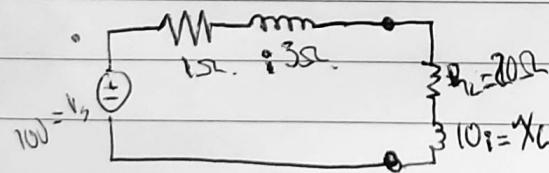

$$100 = I \angle 0^\circ + j3I + 20I \angle 90^\circ + j10I$$

$$I = \frac{100}{21 + j13}$$

$$21 + j13$$

$$I = \frac{100}{21 + j13} \cdot \frac{(21 - j13)}{(21 - j13)} = \frac{100(21 - j13)}{21^2 + 13^2}$$

$$I = 3.44 - j2.13$$

$$I = 5e^{j\theta}$$

$$c = \sqrt{a^2 + b^2}$$

$$I = 4.04e^{j31.8^\circ}$$

$$\theta = \tan^{-1} \left( \frac{b}{a} \right)$$

$$P_{\text{in}} + Q = 171.61$$

$$Q = \frac{1}{2} I^2 R$$

$$Q = \frac{1}{2} I I^* R$$

$$Q = \frac{1}{2} V I^*$$

$$Q = \frac{1}{2} R c [V_{0.2} I^*]$$

$$Q = \frac{1}{2} R c [(0.47e^{j5.2^\circ})(4.04e^{j31.8^\circ})]$$

$$P = \frac{1}{2} Re[365.5 e^{j26.6^\circ}]$$

$$P = 163.41 W$$

$$P_{\text{line}} = \frac{1}{2} I^2 R$$


$$P_{\text{line}} = \frac{1}{2} (4.04)^2 \times 14.04 \Omega$$

$$= 8.2 W$$

$$P_{\text{source}} = \frac{1}{2} Re[V_s I^*]$$

$$P_{\text{source}} = 171.61 W$$

# Transformers

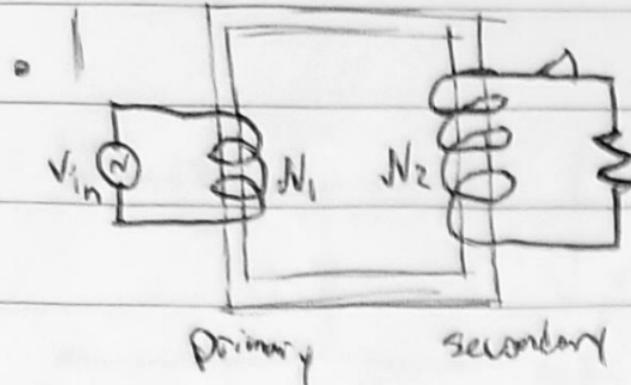

$$\bullet V_{in} = -N_1 \frac{d\Phi}{dt}$$


$$V_{out} = -N_2 \frac{d\Phi}{dt}$$

$$\bullet \frac{V_{in}}{V_{out}} = \frac{N_1}{N_2} \Rightarrow \frac{I_{in}}{I_{out}} = \frac{N_2}{N_1} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{I_{in}}{I_{out}}$$

$\bullet \frac{V_{out}}{V_{in}} = \frac{N_2}{N_1}, N_2 > N_1 \Rightarrow V_{out} > V_{in} \Rightarrow$  step-up transformer

$\frac{V_{out}}{V_{in}} = \frac{N_2}{N_1}, N_2 < N_1 \Rightarrow V_{out} < V_{in} \Rightarrow$  step-down "

# QL Filter

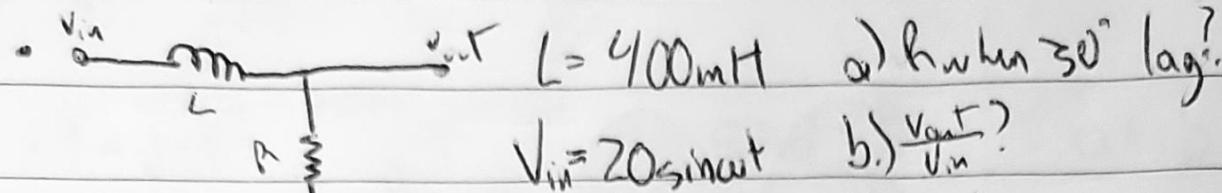


$$\omega = 200 \frac{\text{rad}}{\text{s}} \quad \text{a.) } \frac{V_{out}}{V_{in}} \text{ for swapped R \& L?}$$

$$\tan 30 = \frac{X_L}{V_{out}} = \frac{1 \cdot X_L}{1 \cdot R} = \frac{\omega L}{R}$$


$$R = \underline{\omega L} \quad f = 139 \Omega.$$

$\tan 30$
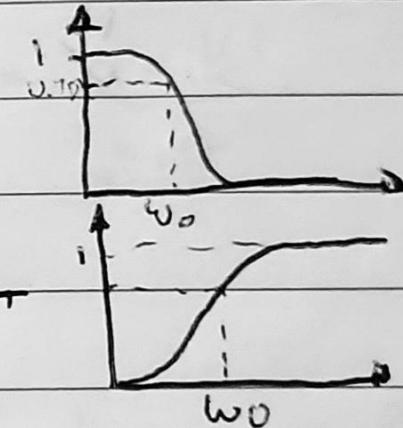
$$\bullet \text{b.) } \frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + X_L^2}} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{R}{\underline{R}} = 1.$$





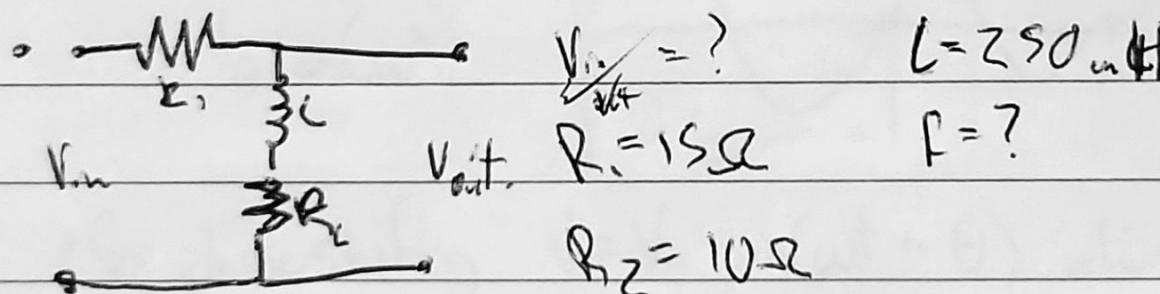
$$\bullet \text{c.) } \frac{V_{out}}{V_{in}} = \frac{1 \cdot X_L}{\sqrt{R^2 + \omega^2 L^2}} = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \approx \frac{1}{\sqrt{1 + \frac{R^2}{\omega^2 L^2}}} = \frac{1}{\sqrt{1 + \frac{f^2}{f_0^2}}} = \frac{1}{\sqrt{1 + \frac{1}{f_0^2 f^2}}}$$




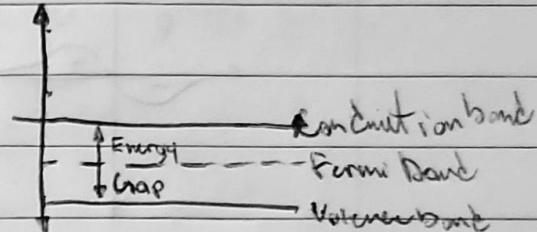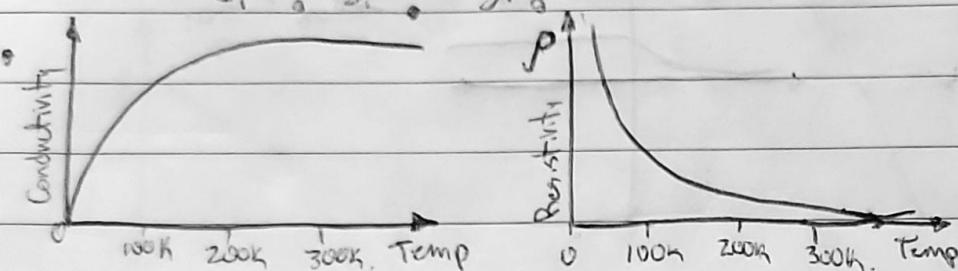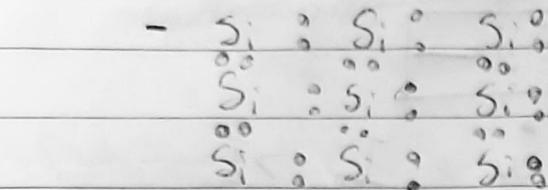
# Semi Conductors

- 2 main elements  $\rightarrow$  Silicon, and Germanium
- In metals each ~~atom~~ atom contributes one free electron
- This ~~is~~ free electron conducts electricity
- In metals there are  $\sim 10^{23}$  free electrons per mole.
- Si, Ge both have 4 valence electrons
  - $\begin{array}{c} \text{Si} & : & \text{Si} & : & \text{Si} & : \\ \text{Si} & : & \text{Si} & : & \text{Si} & : \\ \text{Si} & : & \text{Si} & : & \text{Si} & :\end{array}$



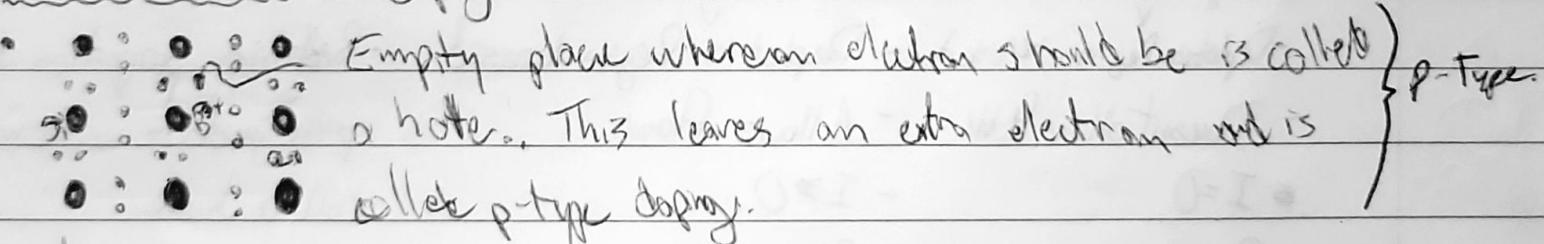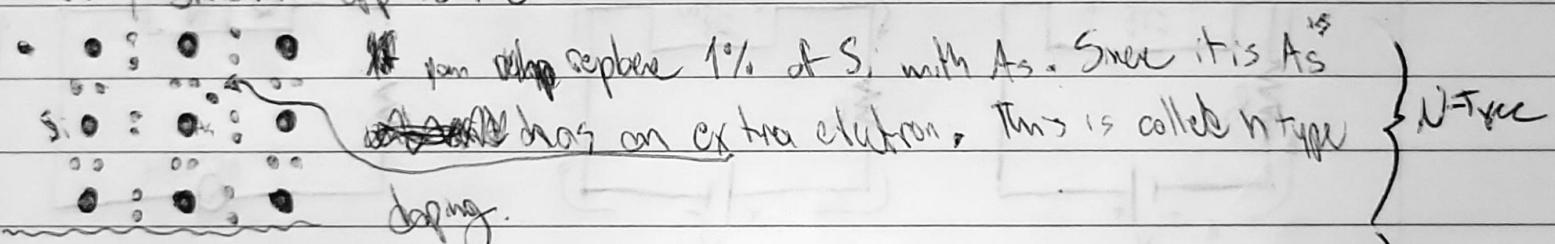- There is conduction due to excitation of electrons by temperature in Si, Ge can carry current which we call is intrinsic current and its very small in applied field.




- $N_c$  is the density of conducting negative electrons,  $n_c \gg n_{int}$

- $N_h$  is the " " " " " hole  $n_h \gg n_c$


- $N_{int}$  " " " " " electrons due to temp.  $n_{int} \gg N_c$
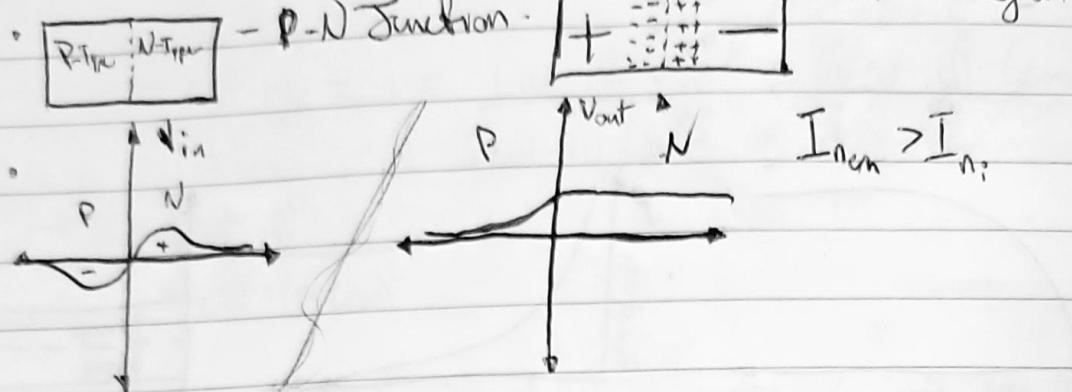
# P-N Junction

- A single crystal of a semiconductor may be grown with acceptor (hole doping) impurities (p-type) or doped with donor impurities (n-type) such that a sharp transition is formed between n & p type material in the crystal.



Forward and Reverse Bias.

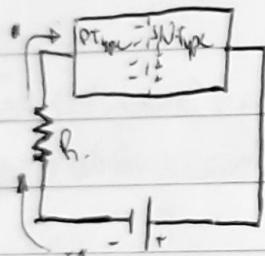

- Depletion region increased

- Doesn't allow flow

$$\bullet I = 0$$


- Reverse Bias

• Symbol =

=

:

Anode      cathode

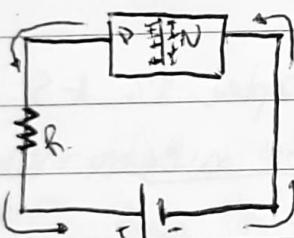


- Depletion region decreased

- Allows flow.


$$\bullet I \geq 0$$

- Forward Bias


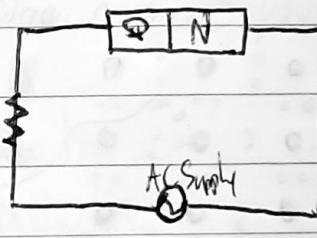


- Rectifier properties of

p-n junction with m  
coll a diode

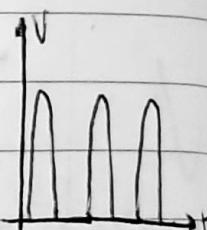

# IV Characteristics

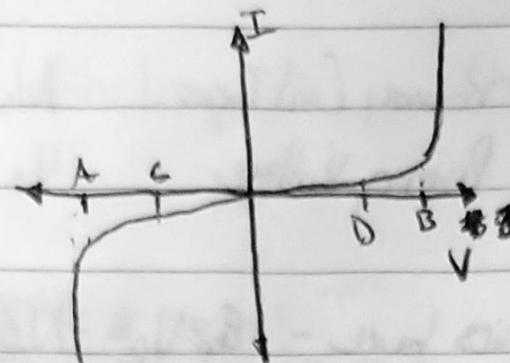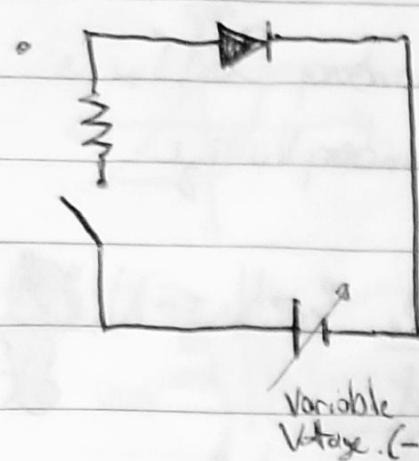


A = Critical Reverse Voltage or  
Breakdown Voltage.

B = Forward Current

C = Reverse Current (Small)

D =  $V_{CUT-OFF}$

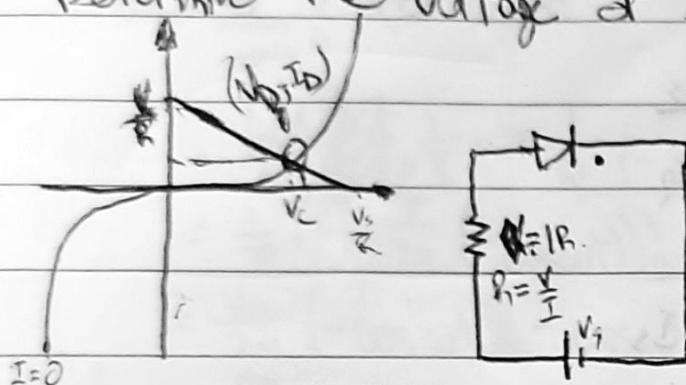- Determine the voltage of I-V for a given Source voltage,  $V_s$ , in forward bias.




$$V_R = V_s - V_D$$

$$I_R = V_s - V_D$$

$$I_R = \frac{V_s}{R} - \frac{V_D}{R}$$

# Transformers

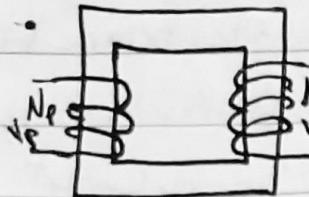

$N_p$  = Primary Coil Turns  
 $V_p$  = Primary Voltage

$N_s$  = Secondary Coil Turns  
 $V_s$  = Secondary Voltage

- Faraday's Law Applies here -  $E_p = V_p = -N_p \frac{d\Phi_p}{dt}$   $E_s = V_s = -N_s \frac{d\Phi_s}{dt}$

- The flux through both coils are identical  $\rightarrow \frac{d\Phi_p}{dt} = \frac{d\Phi_s}{dt}$ .

$$\frac{V_s}{V_p} = \frac{-N_s \frac{d\Phi}{dt}}{-N_p \frac{d\Phi}{dt}}$$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$\text{Input power} = \text{Output Power} \Rightarrow P_p = P_s$$

$$V_p I_p = V_s I_s$$

$$\frac{I_p}{I_s} = \frac{V_s}{V_p} = \frac{N_s}{N_p}$$

- Note: If you need high voltage output, you decrease the output current & vice versa.

- Circuit Symbol -

## Example

$$\begin{array}{c} \text{---} \\ \text{---} \\ \text{---} \end{array} \text{---} \quad V_p = 3600 \text{ V} \quad V_s = 120 \text{ V} \\ N_p = ? \quad N_s = 60 \\ I_p = 3 \text{ A} \quad I_s = ? \end{array}$$


$$\frac{V_s}{V_p} = \frac{N_s}{N_p} \Rightarrow 1800 \text{ turns} = N_p$$

$$I_p = \frac{I_s}{30} \\ I_s = I_p 30$$

# Transformers



Hysteresis Loop.

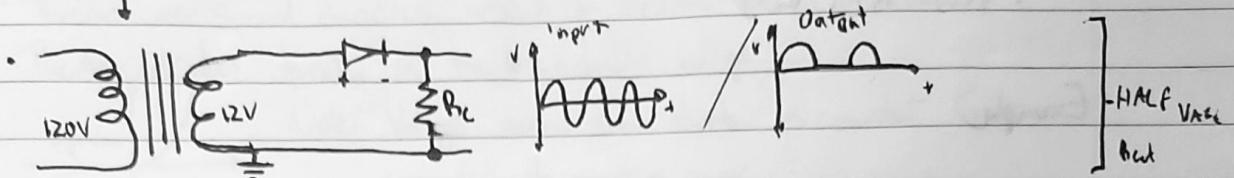

$$V_{AVG} = \frac{1}{T} \int_0^{\frac{T}{2}} V_p \sin \omega t dt$$

$$= \frac{1}{T} \cdot \frac{1}{2\pi} \cdot \frac{1}{2} \cdot V_p \cdot \frac{1}{\omega} \left[ -\cos \omega t \right]_0^{\frac{T}{2}}$$

$$= \frac{1}{T} \cdot \frac{1}{2\pi} \cdot \frac{1}{2} \cdot V_p \cdot \left( -\cos \omega t \right)_0^{\frac{T}{2}}$$



$$= \frac{V_p}{2\pi} \left( -\cos \omega t \right)_0^{\frac{T}{2}} = \frac{V_p}{2\pi} \left( -\cos \omega \frac{T}{2} \right)$$

$$V_{AVG} = \frac{V_p}{\pi}$$



- 0.6 - 0.7 is equivalent to turn on the diode.

$$I_{DC} = \frac{V_{AVG}}{R_L}$$

PT

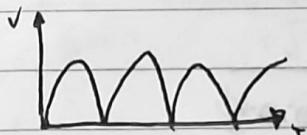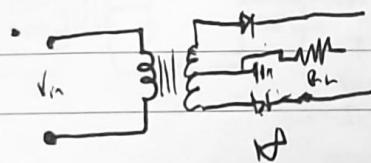


- Full Wave  
Rectifier

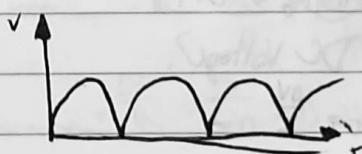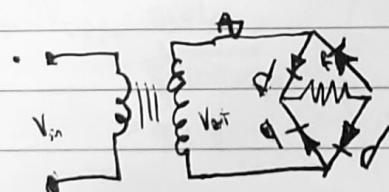

- Full Wave  
Rectifier
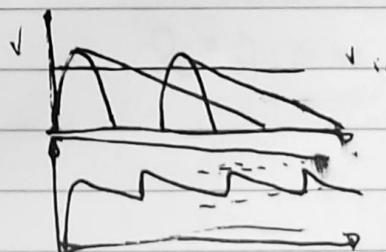
$$\text{- Total required voltage} = 1.4V.$$



- Inductance  
voltage

$$\cdot V(t) = V_0 e^{-\frac{t}{RC}}$$

$$= V_0 \left[ 1 - \frac{t}{RC} + \frac{t^2}{2(RC)^2} - \frac{t^3}{3(RC)^3} \dots \right]$$

- Then we choose an RC such that  $T \ll RC$  so only the first term is needed

$$\cdot V(t) = V_0 \left[ 1 - \frac{t}{RC} \right]$$

Example

- Ripple Voltage

$$\Delta V = V_0 \left[ 1 - \left( 1 - \frac{t}{RC} \right) \right]$$

$$= V_0 \frac{T}{RC} \quad T = \frac{1}{2f}$$

$$\Delta V = \frac{V_0}{2fRC} \quad \left. \begin{array}{l} \text{Full Wave Rectifier} \\ \text{Buck Converter} \end{array} \right\}$$

- For a circuit with  $100\mu F = C$ ,  $2fRC = 60000 \Omega \times 10^{-6} s = 600 \text{ ms}$ ,  $6V_{\text{rms}} = V_s$ ,  $f = 60 \text{ Hz}$

$$\Delta V = \frac{V_s}{2fRC}$$

$$= \underline{\underline{6V_{\text{rms}}}}$$

$$= \frac{2(60)(60000)(10^{-6})}{2(60)(100 \times 10^{-6})}$$

$$= V_{\text{rms}} (\cancel{100000}) = \sqrt{2}(0.088888)$$

$$\Delta V = \cancel{0.088888} \sqrt{0.7} V.$$

- What is the DC Voltage?


$$\cdot V_{\text{DC}} = V_0 - \frac{\Delta V}{2}$$

$$= 8.9 - 0.7$$

$$= 8.05 V$$

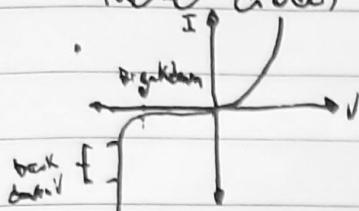
# Zener Diode

- We want a circuit with no ripple voltage ( $\Delta V = 0$ ).
- For this we use zener diodes.
- These are special diodes which can recover from a breakdown.
- These diodes operate in the breakdown voltage.




Note: Voltage across zener diode is constant for any current in its operating range.

Circuit Symbol:

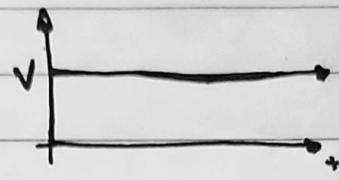

## Example

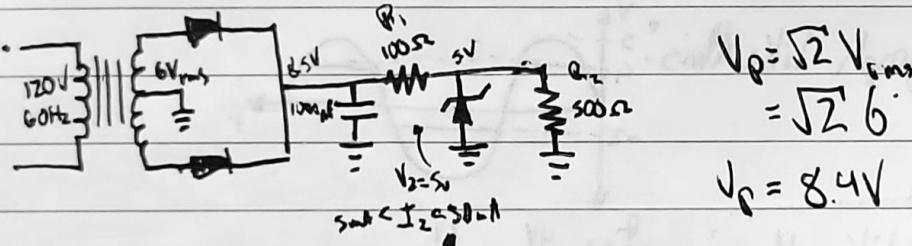

$$V_o = \sqrt{2} V_{rms} = \sqrt{2} 6 = 8.4V$$

$$\text{Stability } \Delta V_{\text{Supply}} = \frac{1}{R_1 R_2 L} \\ = \frac{1}{(100)(100)(1000 \mu F)} \\ = 24 \text{ V}$$

$$I_{\text{reverse}} = I_Z = \frac{\Delta V}{R_1} = \frac{0.5 - 5}{100} = 0.035 \text{ mA}$$

$$I_{\text{forward}} = \frac{\Delta V}{R_2} = \frac{5}{500} = 0.01A = 10 \text{ mA}$$

How do we choose  $R_1$ ?

$$- R_1 = V_{in} - V_Z$$

$$(0.02I_Z + I_{\text{out}})$$


MAX  $I_Z$

$$\left. \begin{aligned} P_Z &= V_Z I_Z \\ &= (5)(0.035) \end{aligned} \right\} \text{Power Across Zener.}$$

$$P_Z = 0.175 \text{ W}$$


# "Transformer" Circuit with Diodes

- This circuit deals with AC current

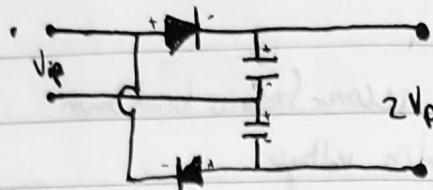


- This is a voltage doubler.

- To quadruple your voltage make this

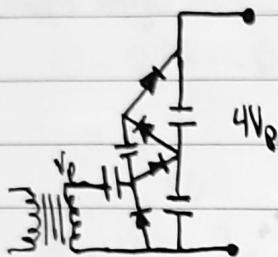


## Cutoff Voltages

- To obtain a graph like this:

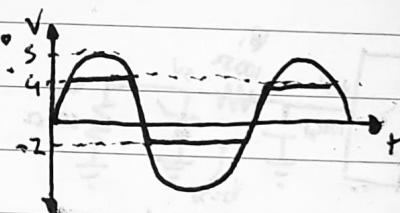

- set up a circuit like this:

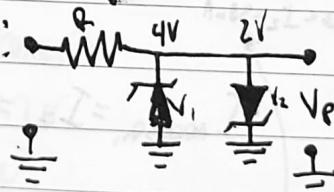


$\frac{6}{2} = 3$

$V_o = \sqrt{2} (2.5 - 0.8)$   
 $\approx 3.5 \cdot 0.6$   
 $\approx 2.1V$

$$I_{DDE} = K e^{\left[ \frac{-e(V_0 - I)}{k_B T} \right]}$$

## Three Terminal Voltage Regulator

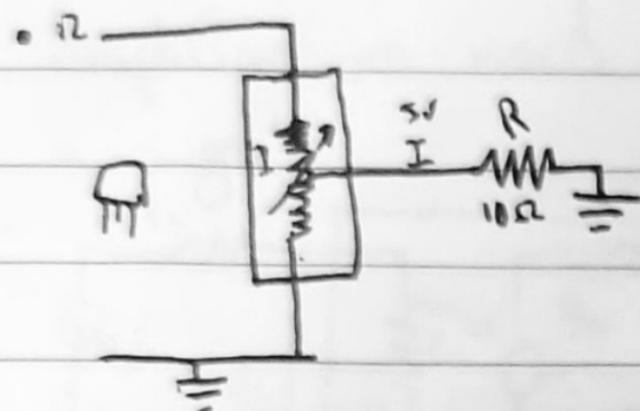

$12 - S = 7$  → Voltage across regulator (variable resistor)

$$\frac{V}{R} = I \Leftrightarrow \frac{S}{10} = I \Leftrightarrow$$


Current in the circuit

$$P = VI \Rightarrow P(0.5) = 3.5W \rightarrow$$

Power used in regulator.
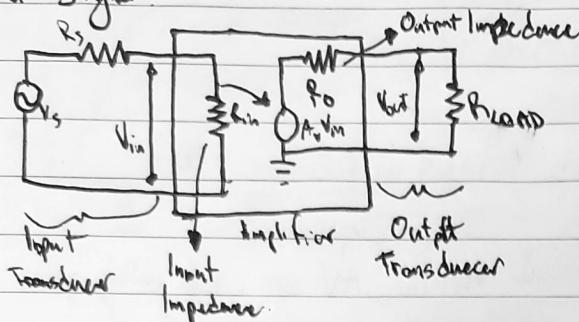
# Amplifiers

- Amplifiers are used to increase the voltage power level of a signal.



$R_{in}$  - Input Impedance

$V_s, R_s$  - Source Voltage / Impedance

$R_L$  - External Circuit Load

$A_v$  - Open Circuit Amplification of Amplifier

$R_o$  = Output Impedance

Example: Microphone -  $R_s = 1000\Omega$       Amplifier -  $R_o = 200\Omega$       Speaker -  $R_L = 8\Omega$

$$V_s = 0.2 \text{ V}_{\text{rms}}$$

$$R_i = 1000\Omega$$

$$A_v = 2000$$

$$V_{in} = \frac{V_s}{R_{in} + R_s} = \frac{0.2}{1000 + 1000} = 0.0182 \text{ V}_{\text{rms}}$$

$$A_v V_{in} = 2000 \cdot 0.0182 = 36.4 \text{ V}_{\text{rms}}$$

$$V_o = A_v V_{in} \frac{R_L}{R_o + R_L} = 36.4 \left( \frac{8}{200 + 8} \right) = 1.4 \text{ V}_{\text{rms}}$$

$$\text{Voltage Amplification} = \frac{V_o}{V_{in}} = \frac{1.4}{0.2} = 7$$

$$P_{out} = \frac{V_o^2}{R_L} = \frac{1.4^2}{8} = 0.245 \text{ W}$$

$$P_{out} = \frac{0.245}{3.6 \times 10^{-6}} = 68600 \text{ W} \quad \text{in dB} \Rightarrow 48 \text{ dB}$$

$$A_p = \text{Power Gain of amp} = \frac{P_{out}}{P_{in}} = \frac{0.245}{3.3 \times 10^{-7}} = 74200 = 58.7 \text{ dB}$$

- There are amplifiers that we call 'voltage follower'.

- This is an amplifier such that the amplification is 1.

- Input impedance =  $\infty$ , Output impedance = load impedance Almost 0




$$V_{in} = V_s \quad R_i = \frac{1}{1 + \frac{R_f}{R_i}} = \frac{1}{1 + \frac{1000}{100}} = \frac{1}{11} = \frac{1}{V_o} \quad R_i^2 = P$$

$$A_V = 1 \quad R_i \left( \frac{1}{11} \right)^2 = P$$

$$P = \frac{(0.2)^2}{8} = P$$

$$V_{out} = A_V \cdot R_L = 0.2 \cdot \frac{R_L}{R_i + R_L} = 0.2 \text{ V} \quad S \times 10^{-8} = P$$

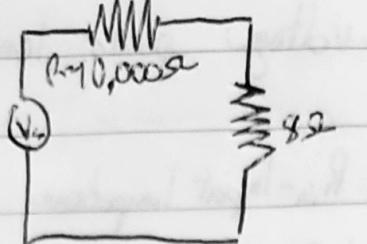- Consider direct connection from Microphone to speaker



$$\begin{aligned} P &= R I^2 \\ &= 8 \left( \frac{1}{10000} \right)^2 \\ &= 3 \times 10^{-9} \text{ W} \end{aligned}$$

Note: Normally  
the output impedance  
of a microphone  
is very small.  
So we can ignore  
it.  
Also, normally  
the input resistance  
of a speaker  
is very large.  
So we can ignore  
it.


- An ideal amp is one with -1- input impedance = 00

2- Output impedance = 0

3- Very large AV open circuit voltage gain
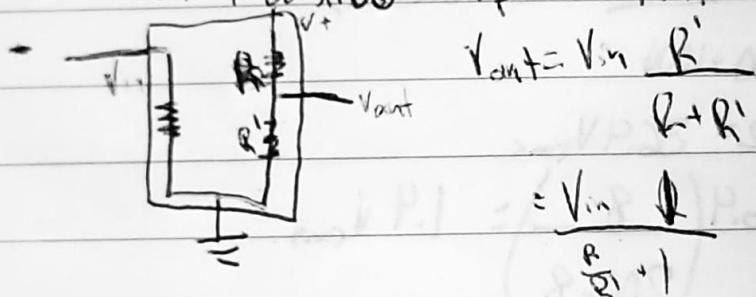
### • Stage Model of Amp

- Transistor or Vacuum tube form an amp
- Amplification is not too high
- Several transistors should be cascaded in order to obtain desired amplification.



$$\begin{aligned} V_{out} &= V_{in} \frac{R_3}{R_1 + R_2} \\ &= V_{in} \frac{R_3}{\frac{R_1}{2} + 1} \end{aligned}$$

- Amplification of stage Amp is low  $\approx$  3-5 times




AC component  
of signal

\* Signal always starts  
DC component within  $V_{\text{supply}}$   
& signal ( $\frac{V_{\text{supply}}}{2}$ )


- Cascade Stage Amp.

# Amplification Bandwidth

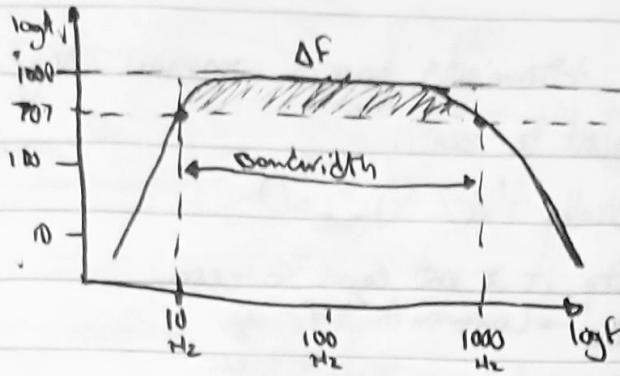

- Any amplifier cannot price to all frequencies. The range of frequencies response of an amplifier is called bandwidth.

## Inverting and Non-Inverting Amplifier

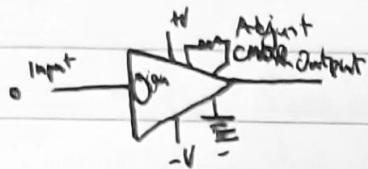

- For inverting amplifier the sign is  $\ominus$
- For non-inverting " " " "  $\oplus$

### Properties

- Inverting  $\rightarrow$


The phase of the output changes by a  $180^\circ$  rotation

Non-Inverting  $\rightarrow$

as the output

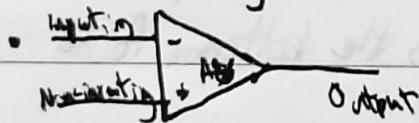
## Difference or Differential Amplifier

- This amplifier has two inputs one inverting and the other non-inverting



$$V_{out} = A_v (V_{in+} - V_{in-}) = A_v V_d$$

### Example

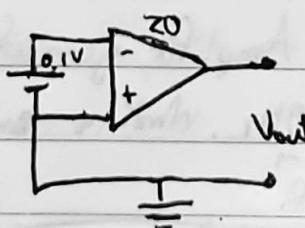


$$V_{out} = A_v (V_{in+} - V_{in-})$$

$$= 20(0 - 0.1)$$

$$V_{out} = -2V$$
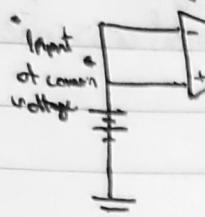
## Real Amplifier

- In real amplifier, when both terminals have common voltage the output voltage is not equal to zero.



Theoretically the  $V_{out} = 0$

- In reality, it is not equal to zero

$$A_{vc} = \frac{V_{oc}}{V_{ic}}$$

$\frac{1}{A_{vc}} = \frac{V_{oc}}{V_{ic}}$

$V_{oc}$  → Common Input Voltage  
 $V_{ic}$  → Common Mode Input Voltage


~~Common Mode Rejection Ratio~~

- CMRR = Common Mode Rejection Ratio =  $\frac{A_{vc}}{A_{vd}}$

$$A_{vd} = \frac{V_{oc}}{V_{id}} \rightarrow \text{Differential Output Voltage}$$

$V_{id} \rightarrow \text{Differential Input Voltage}$

## Johnson Noise

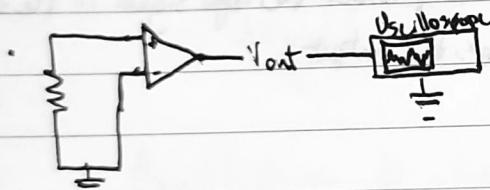


- Johnson noise is the uncertainty created by free electrons inside a resistor

$$P = I_{rms}^2 R = 4K_B T \Delta f, \text{ where } \Delta f \text{ is the bandwidth, } T \text{ is the temperature(K), } K_B \text{ is the boltzmann factor}$$

$$\sqrt{N_{rms}} = \sqrt{4K_B T \Delta f R}$$

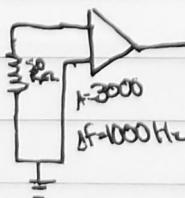- Example → 50 kΩ resistor, 20°C, Amplifier gain of 3000, frequency response of 100 Hz. What is amp output



$$\sqrt{N_{rms}} = \sqrt{4K_B T \Delta f R}$$


$$= \sqrt{4(1.38 \times 10^{-23})(273+20)(100)(50000)}$$

$$\sqrt{N_{rms}} = 0.9 \mu V$$

$$\sqrt{V_{out}} = \pm 0.0027 V$$

$$V_{out} = A_{vd} \sqrt{N_{rms}} = 3000 \cdot 0.9 \mu V = 2.7 mV_{rms}$$

# Operational Amplifier

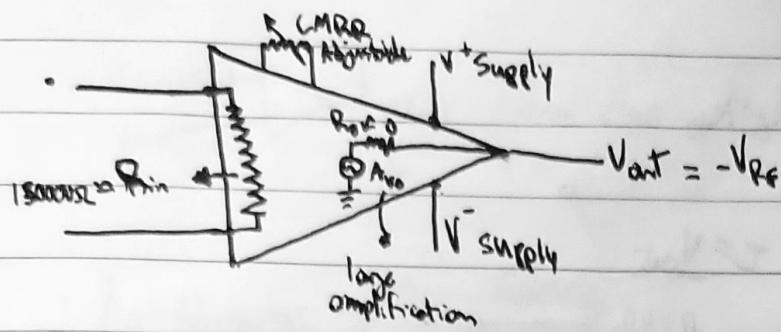


- Inverting Op-Amp



- When the input is connected to the inverting part of amplifier the op-amp is called inverting op-amp

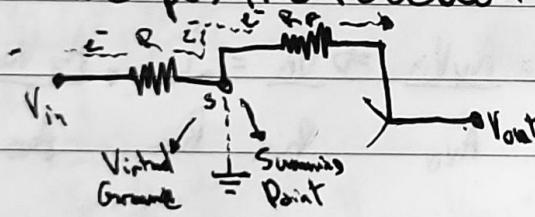- $f_F = \text{Feedback}$
- When the output is connected to  $\ominus$  terminal of op-amp the feedback is called negative feedback
- The positive feedback causes oscillating.



$$\sqrt{R_F} = I_{RF}$$

$$\sqrt{out} = -V_{RF}$$

$$V_{out} = I_{RF}$$


$$V_{out} = \frac{V_{in}}{R_{in}} \cdot R_F$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R_{in}}$$

Notes

- In an op-amp  $V_{out} = A_v \cdot V_{in}$

# Non-Inverting Op-Amp

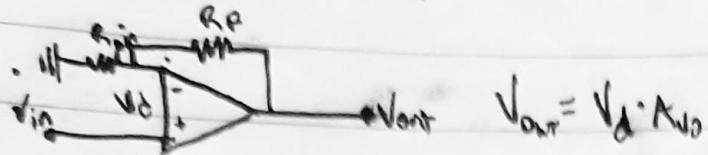

•

$$I = \frac{V_{out}}{R_F}$$

$$I = \frac{V_{in}}{R_L}$$

$$V_{in} = V_d = I R_L = V_{out} \cdot \frac{R_L}{R_F + R_L} \Rightarrow V_{out} = V_{in} \frac{R_F + R_L}{R_L}$$

$$A_V = 1 + \frac{R_F}{R_L}$$

$$A_V = 1 + \frac{15}{3} = 6$$

$$V_{out} = 6V.$$

$$V_{out} = V_{in} \left( 1 + \frac{R_F}{R_L} \right)$$

## • Input Impedance

- This is a very voltage

- 

•


$$V_d = A_V \cdot V_{in} \Rightarrow V_d = \frac{A_V \cdot V_{in}}{A_{vo}} \Rightarrow V_d = \frac{A_V}{A_{vo}} \cdot \frac{V_{in}}{R_{in}} = \frac{1}{A_{vo}} \cdot \frac{A_V}{R_{in}} \cdot V_{in} = \frac{A_V}{A_{vo}} \cdot \frac{V_{in}}{R_{in}}$$

$$I_{in} = \frac{V_{in}}{R_{in}} = \frac{A_V}{A_{vo}} \cdot \frac{V_{in}}{R_{in}} \Rightarrow I_{in} = \frac{A_V}{A_{vo}} \cdot \frac{V_{in}}{R_{in}} \Rightarrow R_{input} = \frac{A_{vo} \cdot R_{in}}{A_V}$$

- Ex.  $A_{vo} \approx 200,000$ ,  $A_V \approx 100$ ,  $R_{in} = 2 M\Omega$ ,

$$R_{input} = \frac{200,000}{100} \cdot 200,000 = 4,000,000 \Omega$$

# Voltage Follower

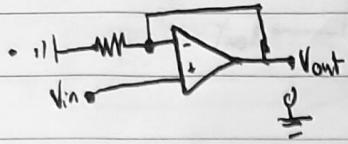


$$\begin{aligned} V_{in} &= V_{out} \text{ by } V_{out} = V_{in} \left(1 + \frac{R_f}{R}\right) \\ &\approx V_{in} \left(1 + \frac{0}{R}\right) \\ &= V_{in}. \end{aligned}$$

- An Advantage of this circuit is input impedance  $\approx R_f \gg \infty$
- It also doesn't need load resistor




# Summing Op-Amp

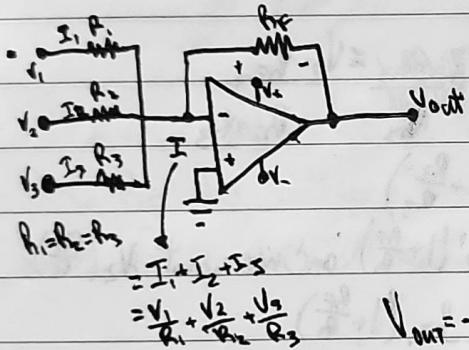


Output signal of  $V_{out} \propto (V_1 + V_2 + V_3)$


$$\begin{aligned} V_{out} &= -V_{RF} = I R_f \\ &= \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right) R_f \\ &= (V_1 + V_2 + V_3) \frac{R_f}{R} \quad \text{if } R_1 = R_2 = R_3 = R \\ V_{out} &= (V_1 + V_2 + V_3) \quad \text{if } R_f = R \end{aligned}$$

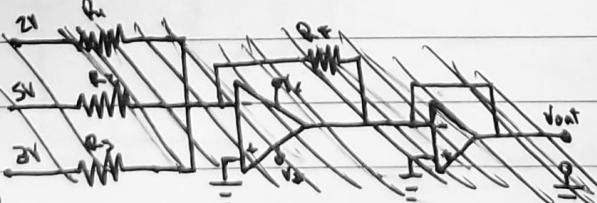Design Summing Device to add 3 Volts ( $V_1 = 2V$ ,  $V_2 = 5V$ ,  $V_3 = 3V$ )



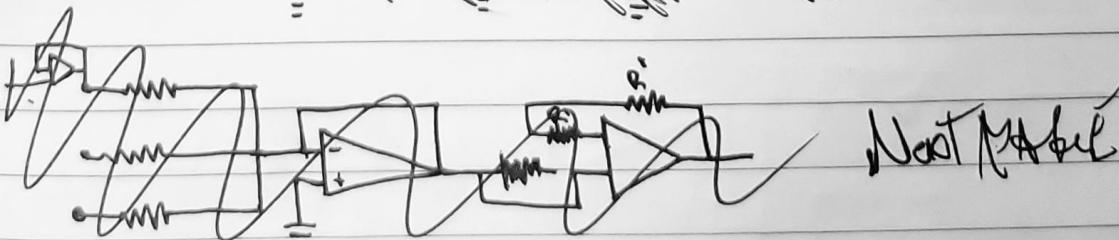
$$\begin{aligned} R_1 + R_2 + R_3 &= R \\ V_{out} &= (V_1 + V_2 + V_3) \cdot A \cdot R_f \end{aligned}$$



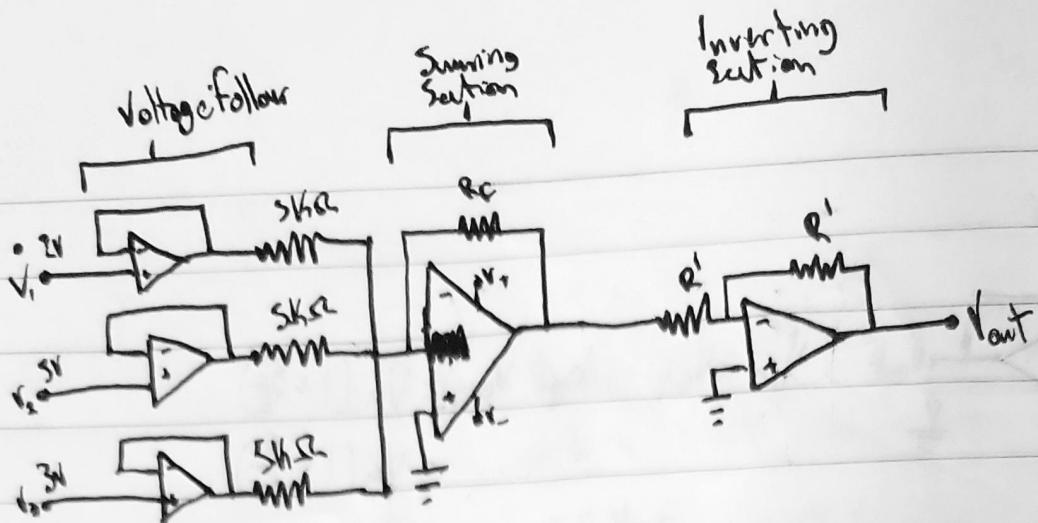


## Difference Op-Amp

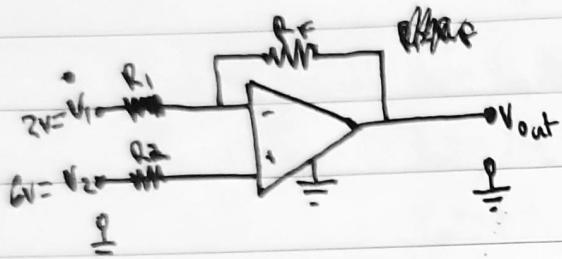

$$V_{out} = V_1 \left( -\frac{R_f}{R_1} \right) + V_2 \left( 1 + \frac{R_f}{R_1} \right)$$

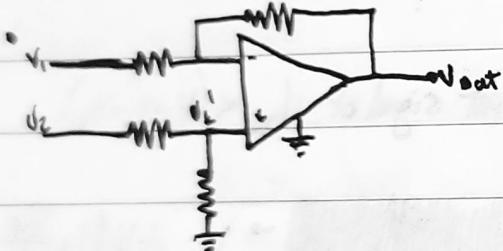~~$R_2 = R_1$~~   
We need to get  $V_{out} = V_1 + V_2$



~~$V_2' = V_2 / (R_2 + R_3) \approx V_2 \frac{R_3}{R_2 + R_3}$~~

$$V_2 = V_2' \left( 1 + \frac{R_3}{R_2} \right)$$

~~$V_{out}(1) = V_1 + V_2'$~~   $V_{out}(1) > V_2' \left( 1 + \frac{R_3}{R_2} \right)$  and we want  $V_2 \left( \frac{R_3}{R_2} \right)$


$$= V_2 \frac{R_3}{R_2} \left( 1 + \frac{R_3}{R_2} \right)$$

$$\frac{R_f}{R_2} = \frac{R_3}{R_2}$$


$$\frac{R_f}{R_2} = \frac{R_3}{R_2 + R_3}$$

$$\frac{R_2 + R_3}{R_2}$$

$$= V_2 \left( \frac{R_3}{R_2} \right)$$

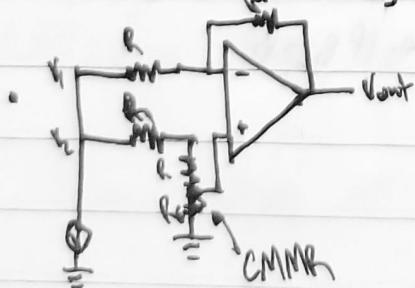


## Constant Current Source.

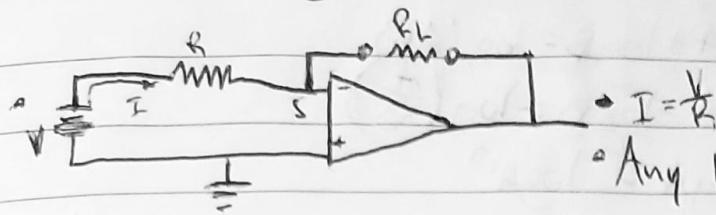

$$I = \frac{V}{R}$$

Any load will receive constant current.

- Current to voltage converter

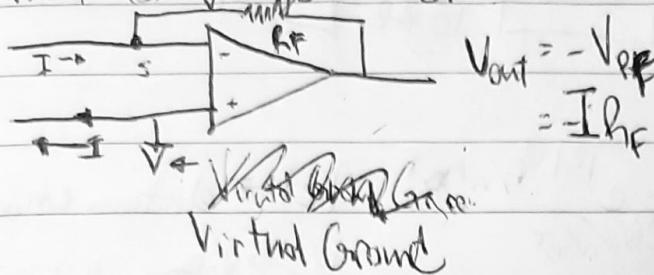

## Example

- Voltmeter reads Volts, construct an ammeter that reads 10  $\mu$ A, find  $R_f$  also, voltage that appears between the microammeter leads if you run 741 op-amp,  $V_{out} = 1V$  micro ammeter

$$V_{out} = -IR_f$$


$$1V = |I| R_f$$

$$1V = |I| R_f \quad 10 \mu\text{A} = |I|$$

$$V_{out} = V_o A_{v,0}$$


$$1 = V_o 20000$$

$$R_f = 1M \quad 5V = V_o$$

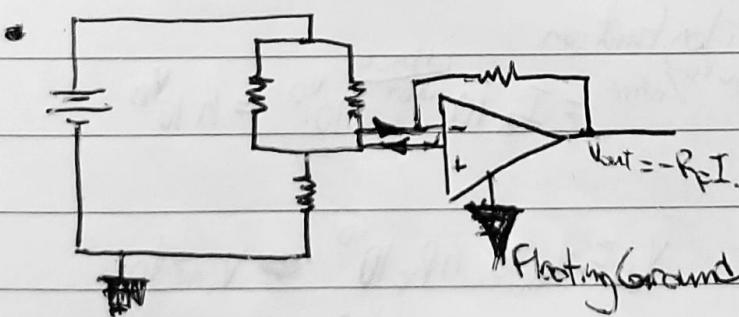
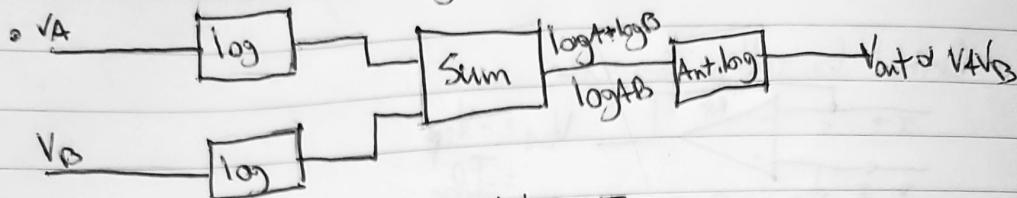
## Logarithmic Function Block.



- we know -  $\log A + \log B = \log (AB)$
- $\log A - \log B = \log \left(\frac{A}{B}\right)$
- $n \log A = \log A^n$



$I = I_D e^{\frac{eV_D}{nK_B T}}$        $I_D = e^{\frac{eV_B}{nK_B T}}$        $I_R = e^{\frac{e(V_D - V_B)}{nK_B T}}$

$$\log \frac{I_R}{I_D} = \log \frac{e^{\frac{e(V_D - V_B)}{nK_B T}}}{e^{\frac{eV_B}{nK_B T}}} = \frac{e(V_D - V_B)}{nK_B T}$$
 $V_D = 0.0059 n \log \left( \frac{I_R}{I_D} \right)$ 

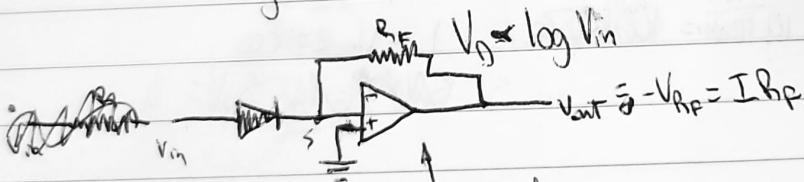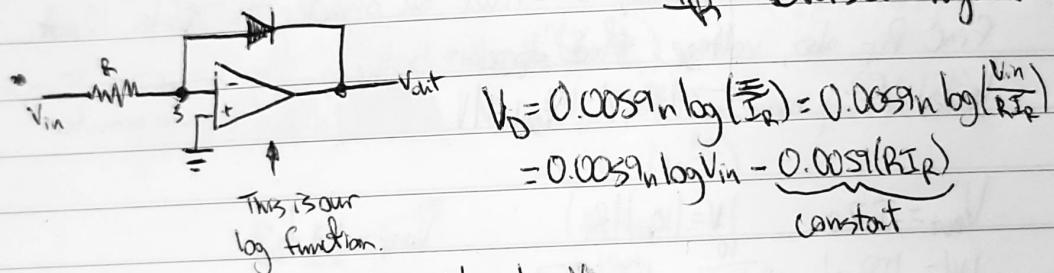$I_D \rightarrow$  electron charge  
 $V_D \rightarrow$  Voltage across diode  
 $n \rightarrow$  Fudge Factor ( $\frac{S_i - 1}{G_i - 2}$ )  
 $k_B \rightarrow$  Boltzmann Factor  
 $T \rightarrow$  Absolute temperature  
 $I_D \rightarrow$  reverse leakage voltage




$$I = I_D \exp \left[ \frac{eV_D}{nK_B T} \right] = I_D 10^{\frac{e(V_D - V_B)}{nK_B T}} = I_D 10^{\frac{e(V_D - V_B)}{nK_B T}} 10^{\frac{eV_B}{nK_B T}} = K 10^{V_D}$$


$$V_{RF} = I_R R_F = K 10^{V_D} R_F$$

$$V_{out} = -V_{RF} = K R_F 10^{V_D} \Leftrightarrow V_{in} = V_D$$


$$= K R_F 10^{V_D}$$

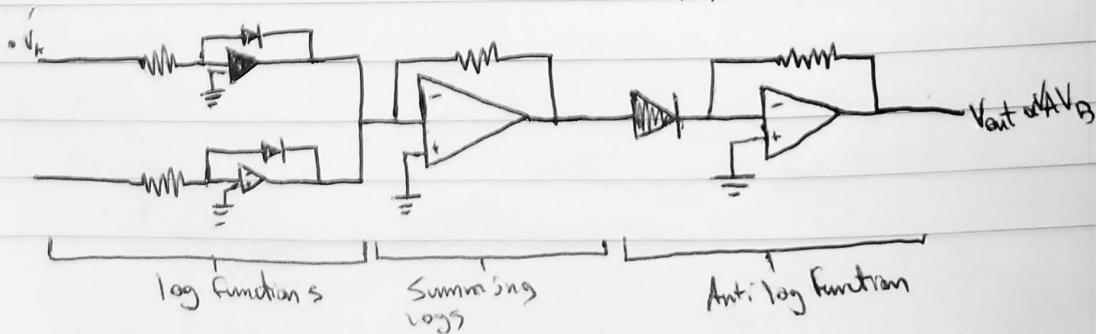

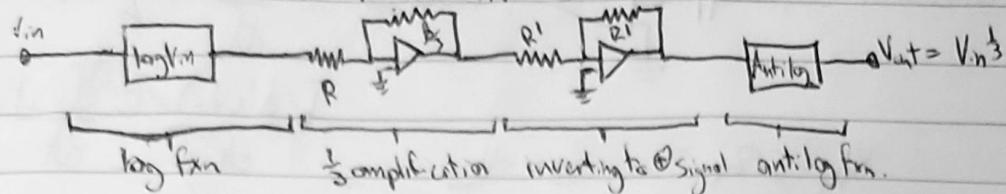- Make a circuit with  $V_{out} = V_{in}^{\frac{1}{3}}$



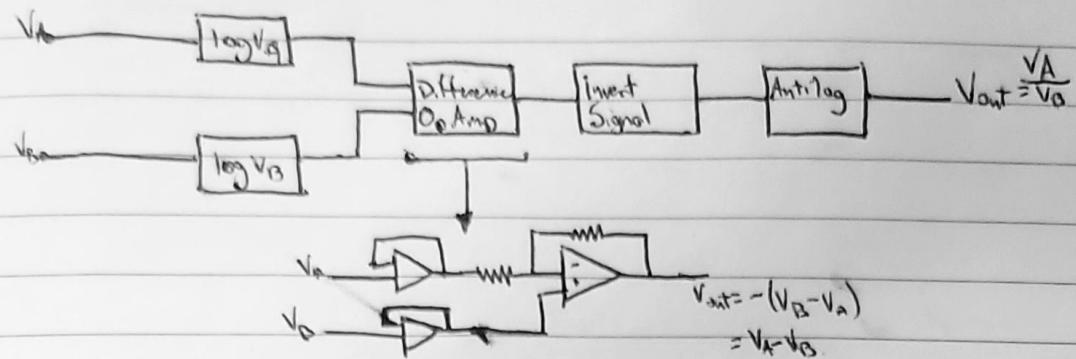- Make a circuit with  $V_{out} = \frac{V_A}{V_B}$




## Differential and Integrating Circuits

•  $q = VC$      $I = \frac{dq}{dt}$      $\Rightarrow I dt = \frac{dq}{dt} dt$   
 $\int_{t_0}^t I dt = \int_{q_0}^q dq$   
 $\int_{t_0}^t I dt = \int_{q_0}^q dq$   
 $\int_{t_0}^t I dt = q$

when  $t=t_0 \Rightarrow q_0 = 0$ ,  
 $t_0 = 0$

Note:  
If  $V_{in}$  is constant  
 $V_{out} = \frac{V_{in}}{RC}$

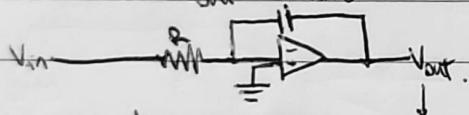We want  $V_{out} \propto \sqrt{V_{in} dt}$




$$I = \frac{V_{in}}{R} \quad I = \frac{dq}{dt} \Rightarrow \int_{t_0}^t dq = \int_{0}^t I dt$$

$$q - q_0 = \int_{t_0}^t \frac{V_{in}}{R} dt$$


$$q = \int_{t_0}^t V_{in} dt \quad q = \frac{1}{2} C V_{in} t$$

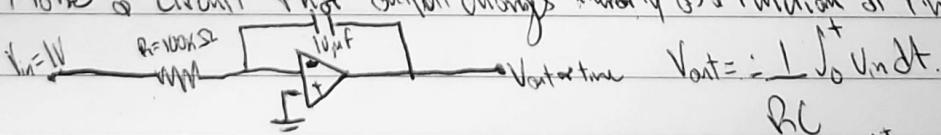- Make a circuit that output charge linearly as a function of time




$$= \frac{1}{(100 \times 10^3)(10^{-6})} \int_{0}^t V_{in} dt$$

$$V_{out} = + \frac{Volts}{seconds}$$

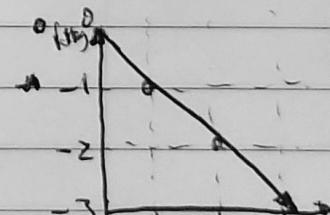

Differentiation

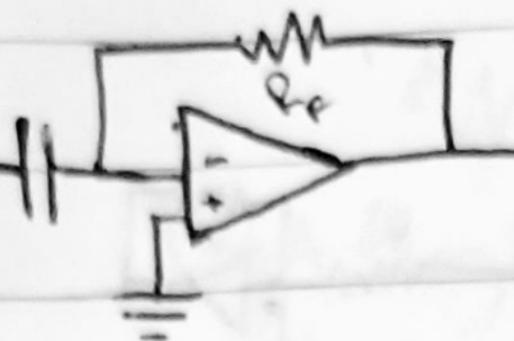

$$I = \frac{dq}{dt} \quad q = CV_{in}$$

$$I = \frac{d(CV_{in})}{dt} = C \frac{d(V_{in})}{dt}$$

$$V_{RF} = IR_F \\ = \frac{C d(V_{in})}{dt} R_F$$

$$V_{RF} = -V_{out} \\ = -C R_F \frac{dV_{in}}{dt}$$